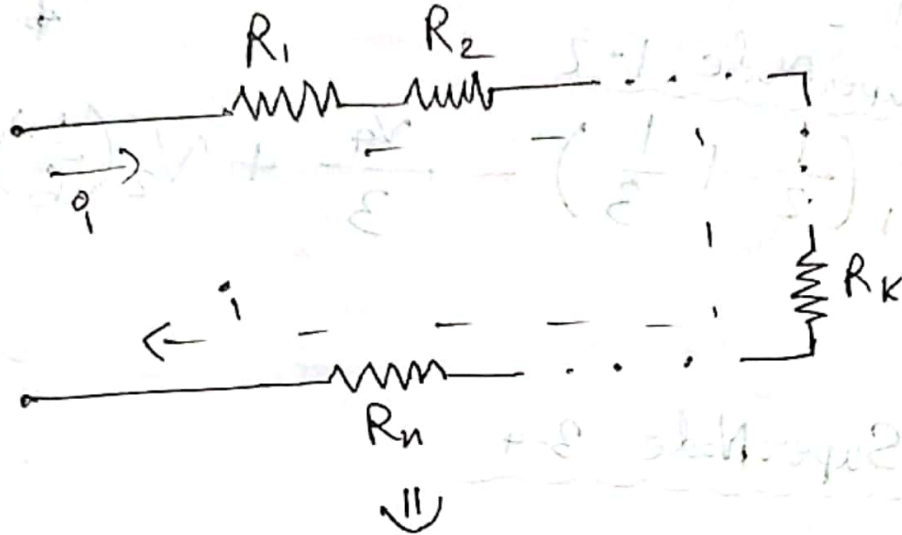


Lecture - 9: Circuit Simplification


Series-Parallel Review

Series



$$R_{eq} = R_1 + R_2 + \dots + R_k + \dots + R_n$$



Parallel

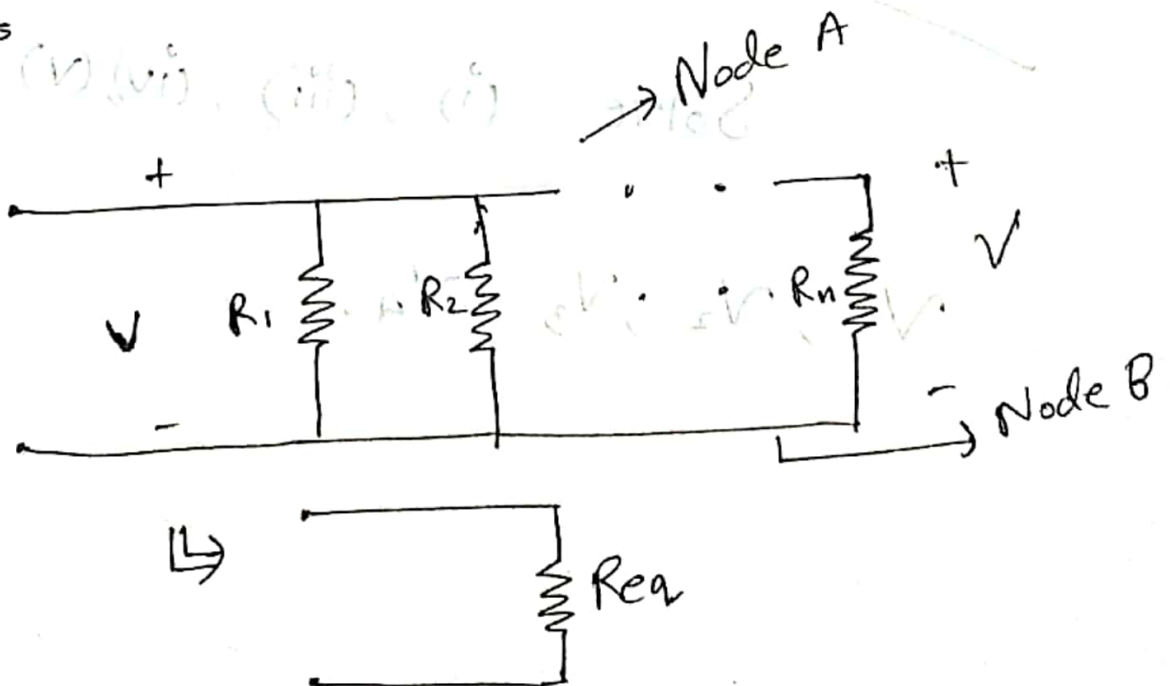

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$


↓
 $R_{eq} \Leftrightarrow R_p$

Example Problem

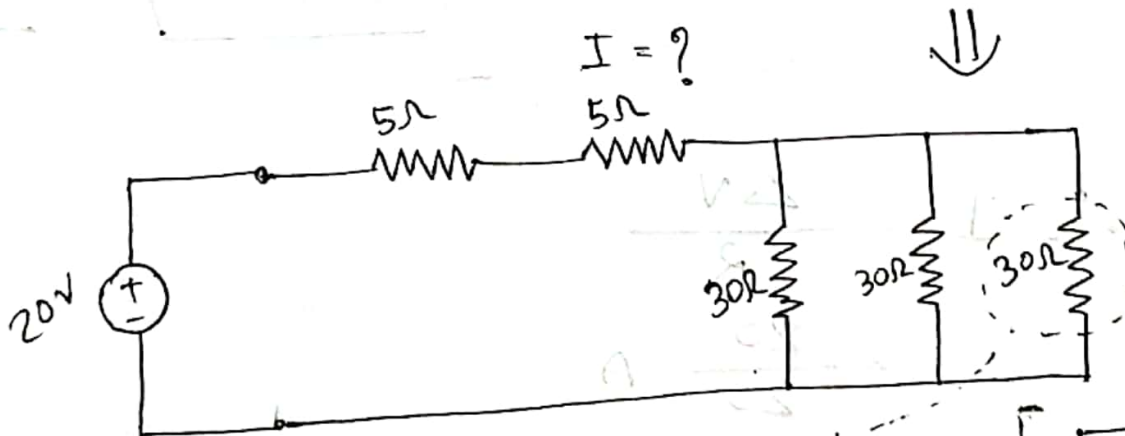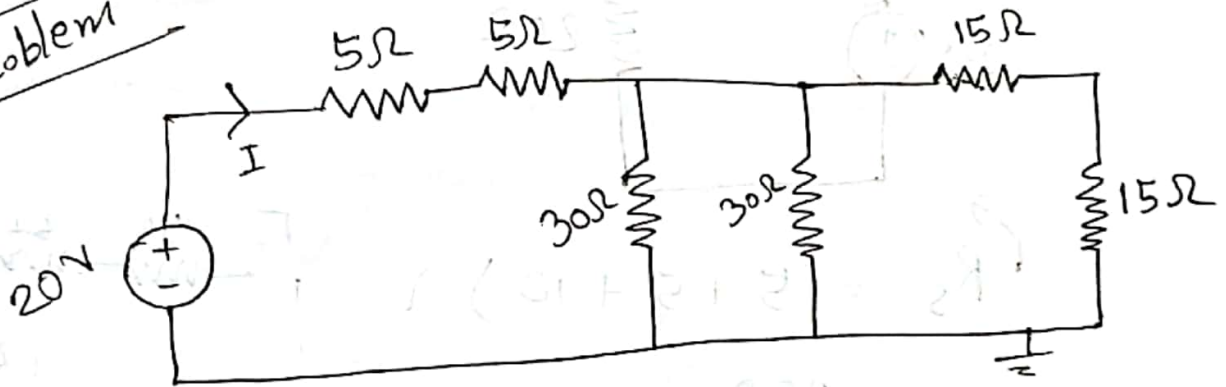


$R_3 = 15\Omega + 15\Omega = 30\Omega$

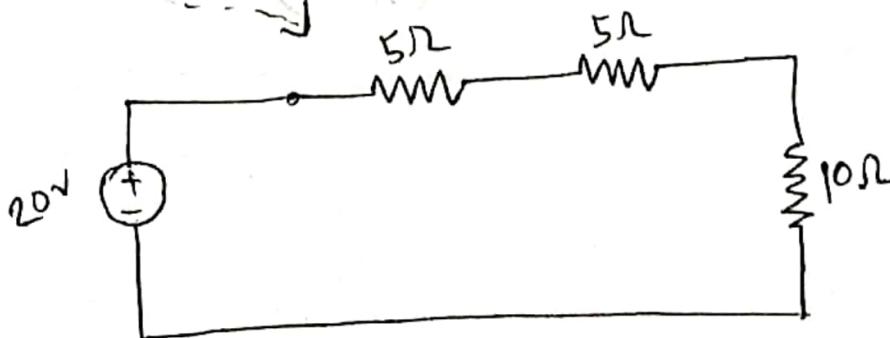
The diagram shows a dashed box around the third parallel branch of the previous circuit. To the right, a separate diagram shows a 15Ω resistor in series with another 15Ω resistor, which is then simplified to a single 30Ω resistor. An arrow points from this simplified 30Ω resistor back to the dashed box in the main circuit diagram.


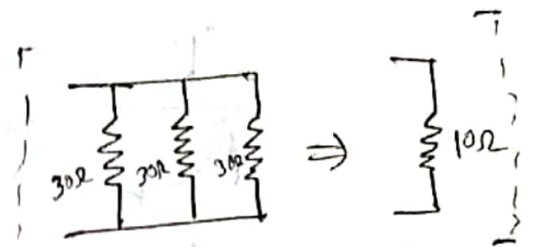
$$\frac{1}{R_p} = \frac{1}{30} + \frac{1}{30} + \frac{1}{30}$$




$$\rightarrow R_p = 10 \Omega$$

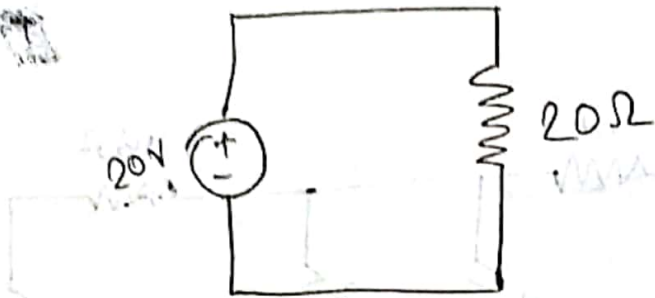

$$R_s = (5 + 5 + 10) \Omega$$

$$= 20 \Omega$$

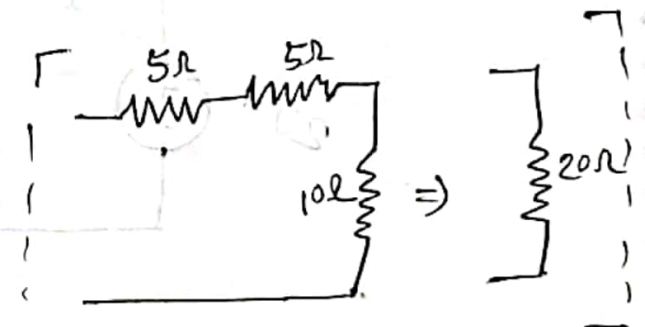

$$I = \frac{\Delta V}{R}$$







$$= \frac{20}{20} \text{ A}$$

$$= 1 \text{ A}$$



(Ans.)

Source Transformation

I-V Characteristics

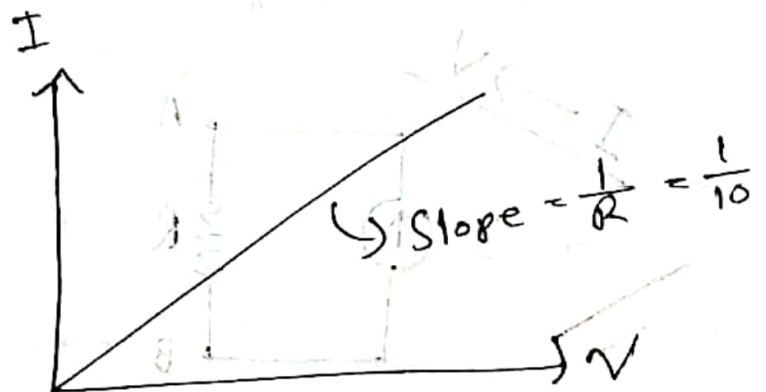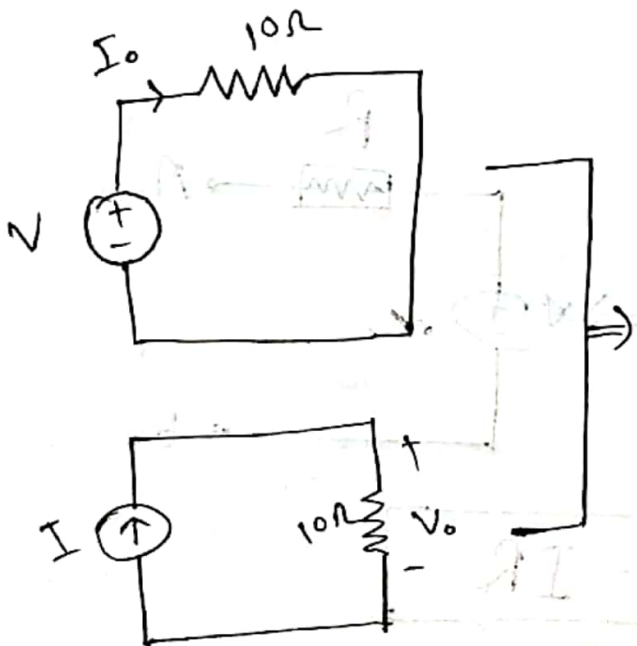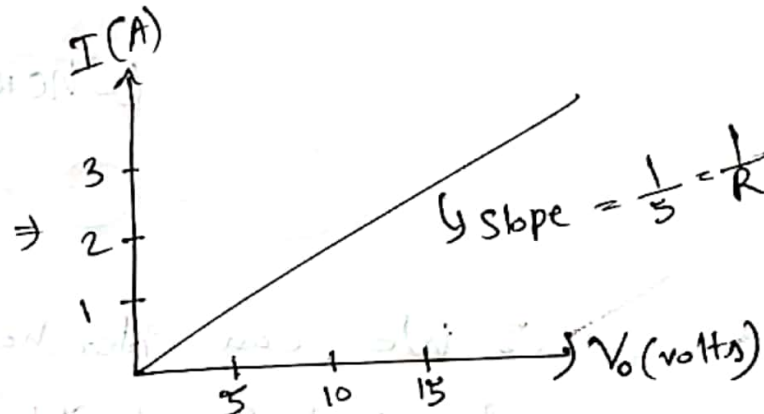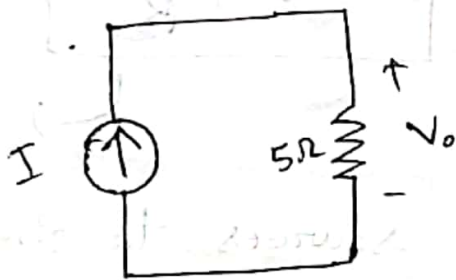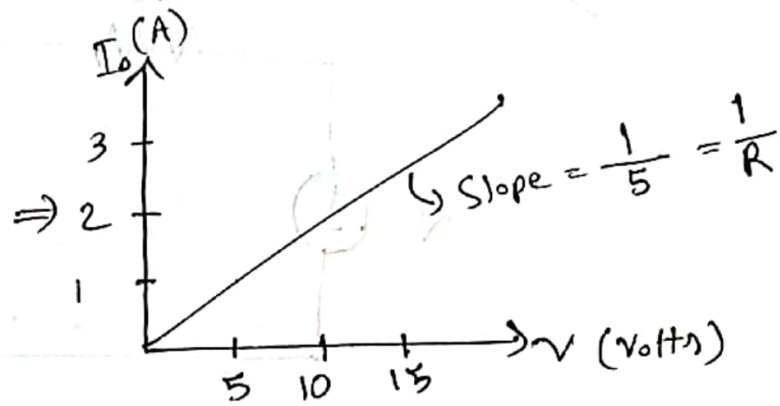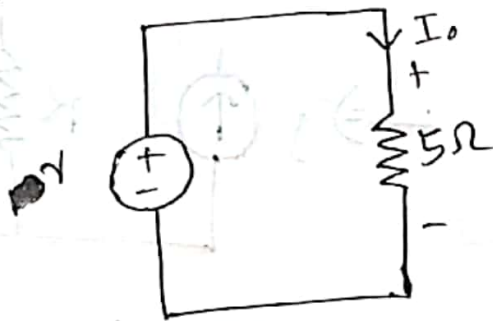

$$\underline{V \rightarrow I}$$

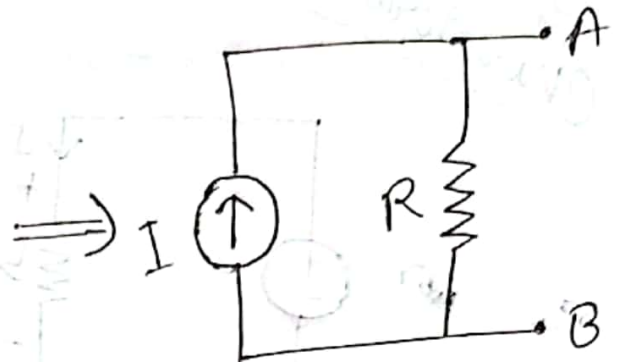
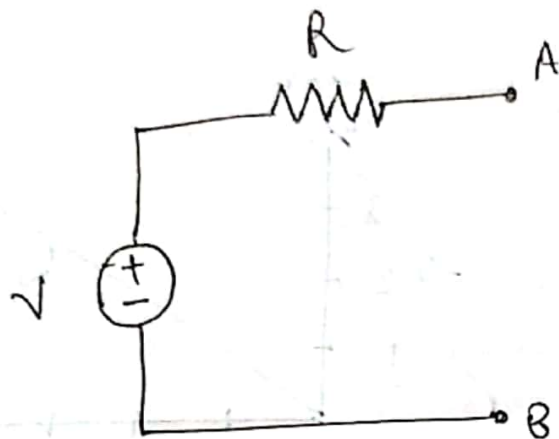


Where, $I = V \cdot \frac{1}{R} = \frac{V}{R}$

↘ Slope




\therefore We can interchange sources to simplify circuit using that formula. The rest of the circuit will be the same.

$$\underline{I \rightarrow V}$$

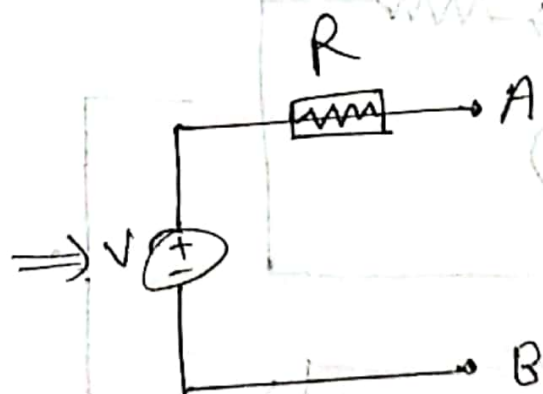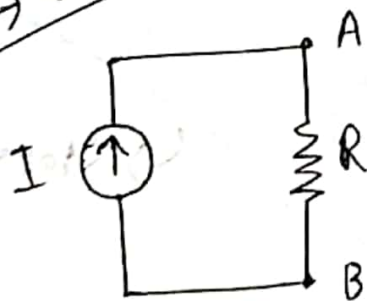


Where, $V = IR$

Signs

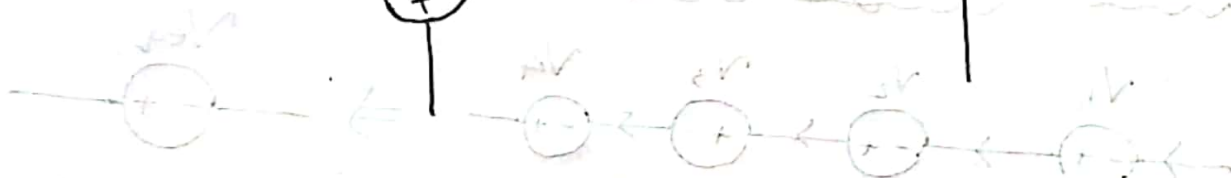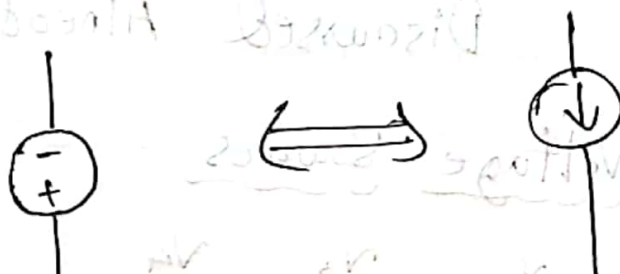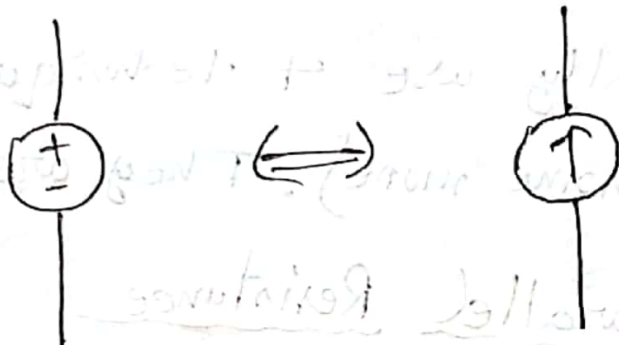

Ex.

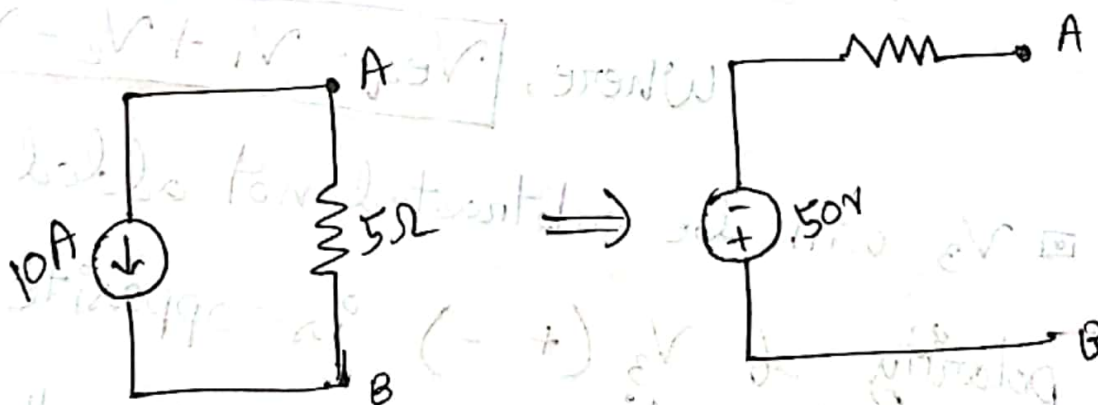


Circuit Simplification Techniques

We basically use 4 techniques (later on we may discuss some more). They are:

1. Series-Parallel Resistance



Discussed Already

2. Series Voltage Sources

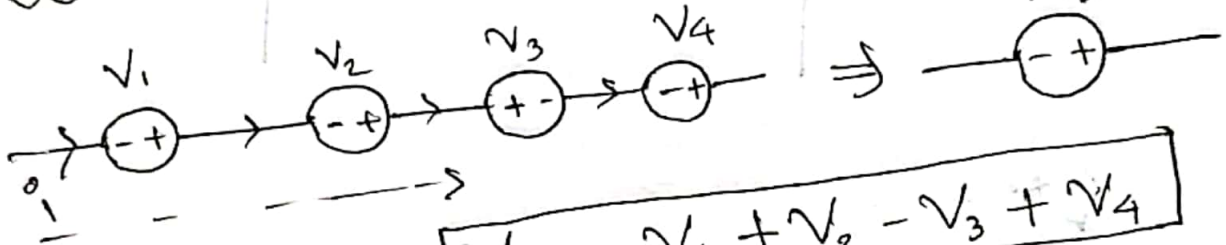

Where, $V_{eq} = V_1 + V_2 - V_3 + V_4$

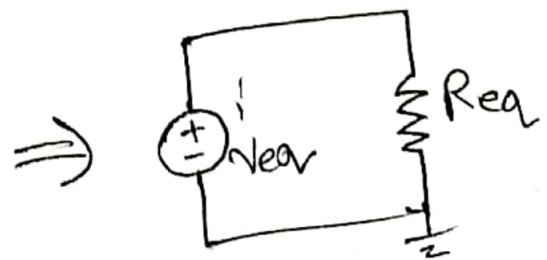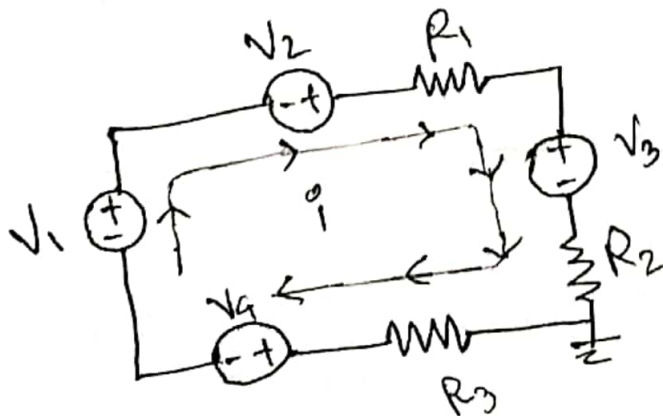
□ V_3 will be subtracted, not added, because the polarity of $V_3 (+ -)$ is opposite of the polarity of $V_{eq} (- +)$. [Polarity with respect to the direction of current $i (- \rightarrow)$]




Where, $V_{eq} = V_1 + V_2 - V_3 - V_4$ V_3, V_4 negative due to their polarity w.r.t current.

$R_{eq} = R_1 + R_2 + R_3$ | Series Resistance |

Common Mistakes

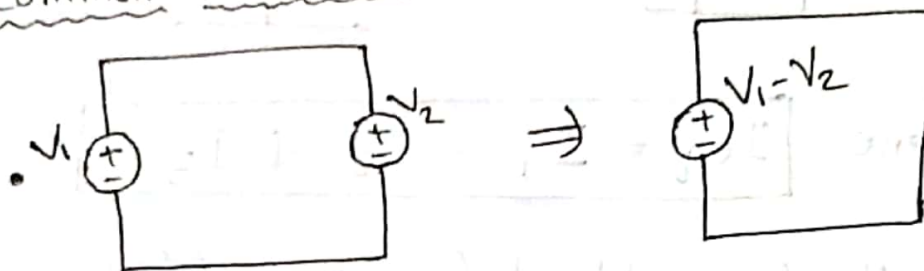

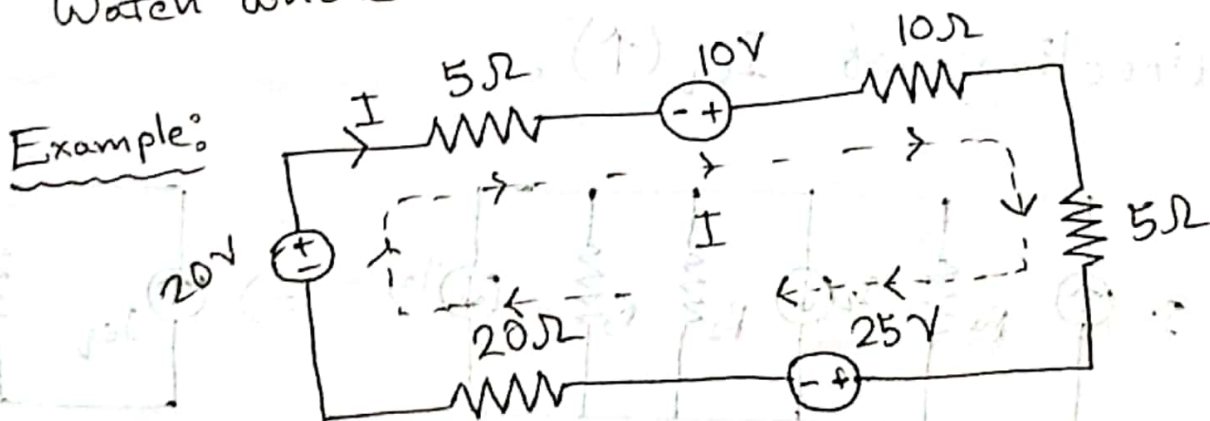Here, $V_{eq} = V_1 - V_2$, not $V_1 + V_2$.
Watch where the current is entering from.



$I = ?$

Here, $V_{eq} = (20 + 10 - 25) \text{ V} = 5 \text{ V}$

$R_{eq} = (5 + 10 + 5 + 20) \Omega = 40 \Omega$




$\therefore I = \frac{V}{R} = \frac{5}{40} \text{ A} = \boxed{0.125 \text{ A}}$

P.S: Watch video for verification


(Am.)

3. Parallel Current Sources

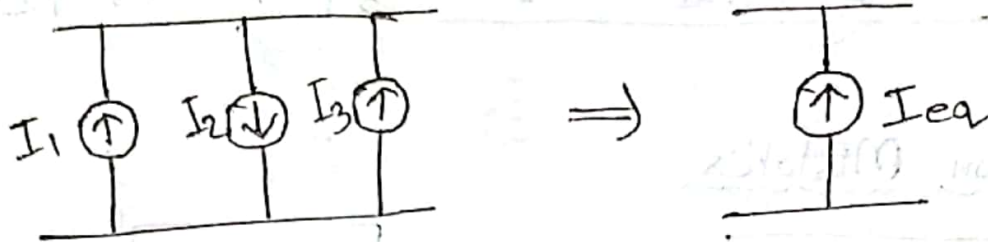

where, $I_{eq} = I_1 - I_2 + I_3$

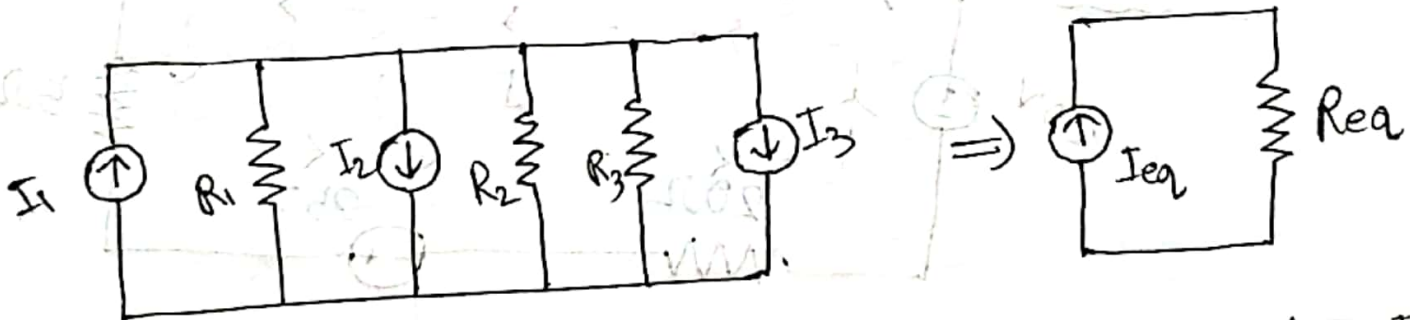□ I_2 will be subtracted, not added, because the direction of I_2 (\downarrow) is ^{the} opposite of the direction of I_{eq} (\uparrow).




where, $I_{eq} = I_1 - I_2 - I_3$

Direction of I_2, I_3 downwards, I_{eq} upwards


$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$ Parallel Resistance

Common Mistakes:

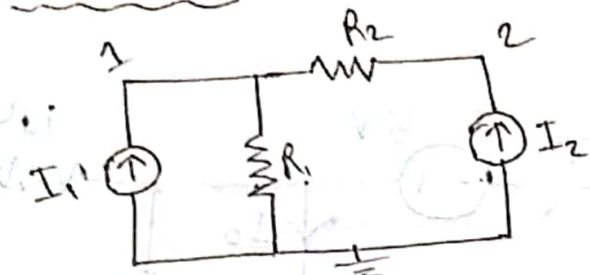

\Rightarrow Here, you can't add I_1 & I_2 simply. Because they don't have the same nodes across them. Hence, they're not parallel.

Example:

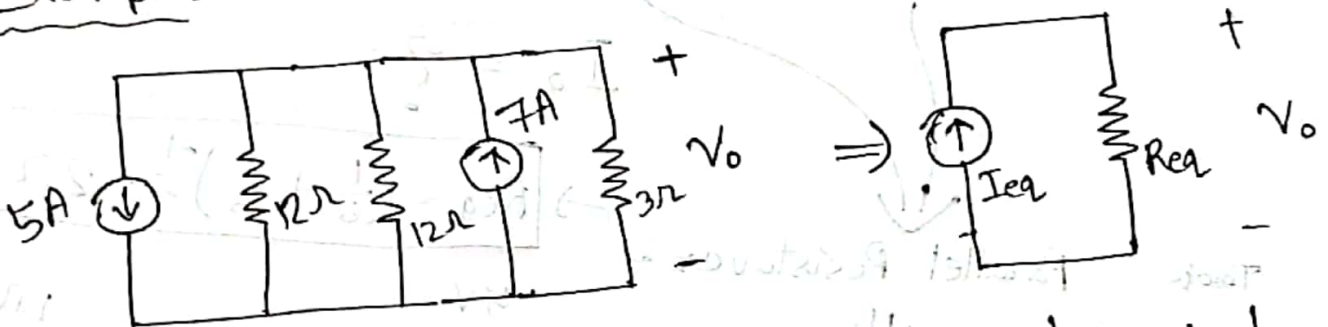

Here, $I_{eq} = -5A + 7A = 2A$ | $I_1 \Rightarrow \downarrow$
 $I_{eq} \Rightarrow \uparrow$

$$R_{eq} = \left(\frac{1}{12} + \frac{1}{12} + \frac{1}{3} \right)^{-1}$$

$$= \left(\frac{1}{2} \right)^{-1}$$


$$= 2\Omega$$

$$\therefore V_0 = IR = I_{eq} \cdot R_{eq} = (2 \times 2) V$$
$$= \boxed{4V}$$

4. Source Transformation

Already discussed.


Example
for ST full problem

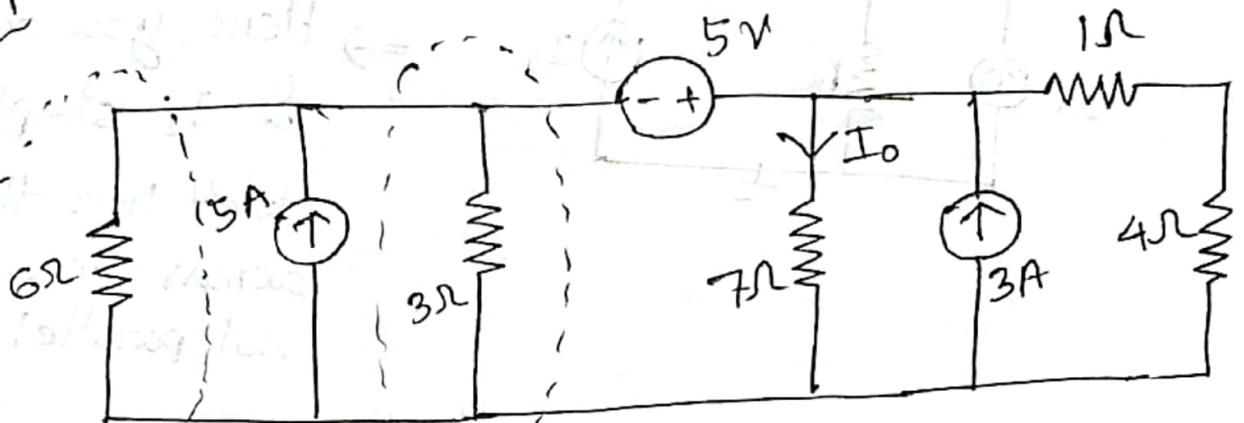

$$I_0 = ?$$


Parallel Resistance
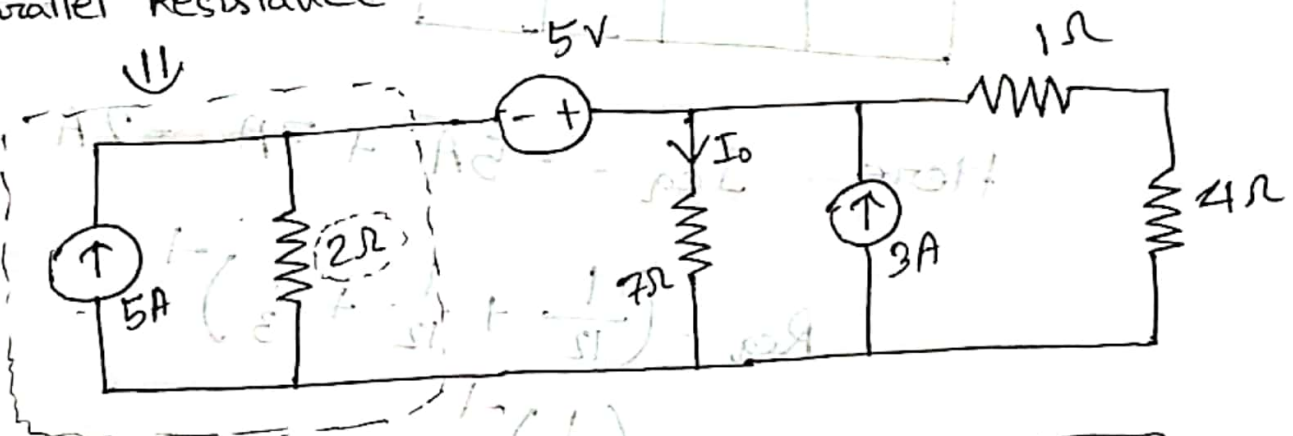
$$R_{eq} = \left(\frac{1}{6} + \frac{1}{3} \right)^{-1} \Omega = 2\Omega$$



$$V = IR = 5 \times 2 \text{ V} = 10\text{V}$$

Source Transformation

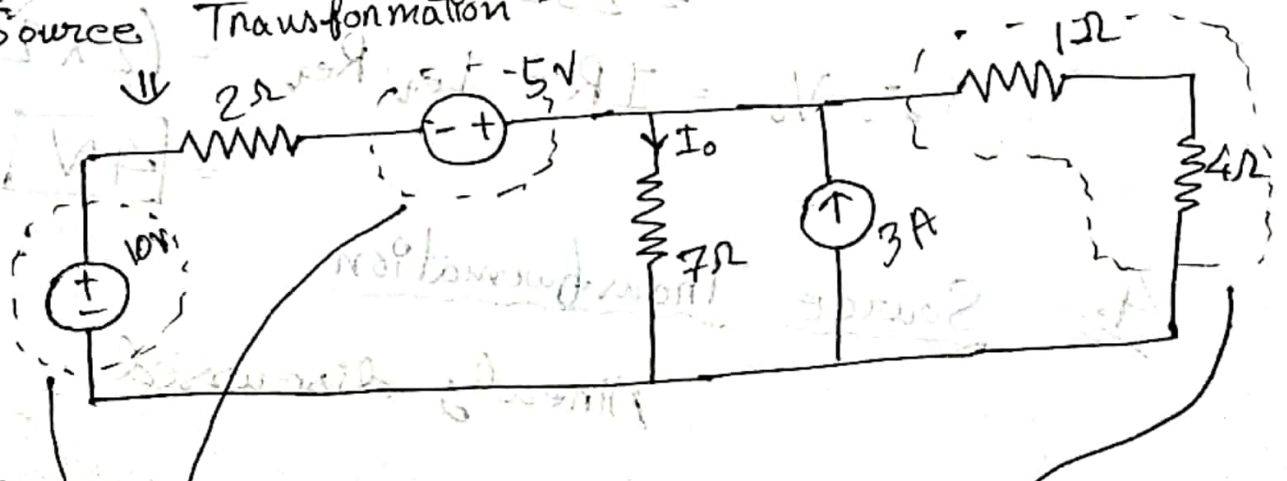


$$V_{eq} = (10 + 5) V = 15V$$

Series Voltage Source


Series Resistance

$$R_{eq} = (1 + 4) \Omega = 5\Omega$$

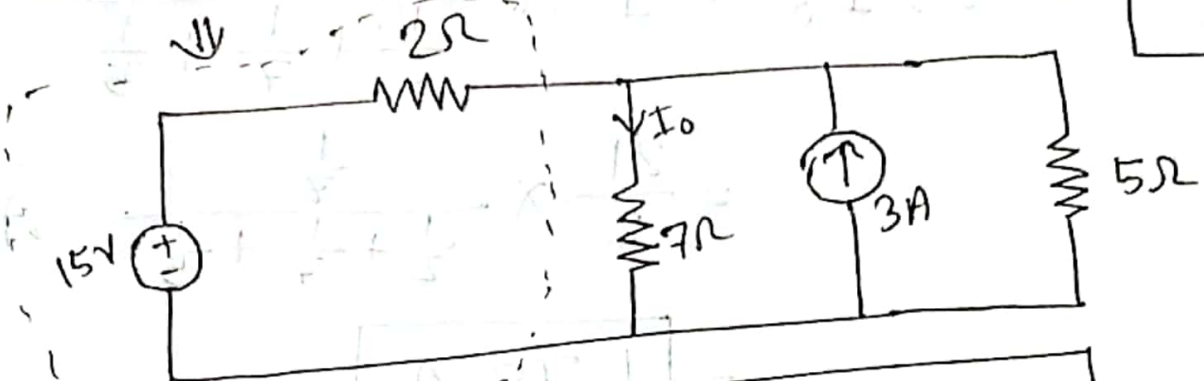


$$I = \frac{V}{R} = \frac{15}{2} A$$

Source Transformation

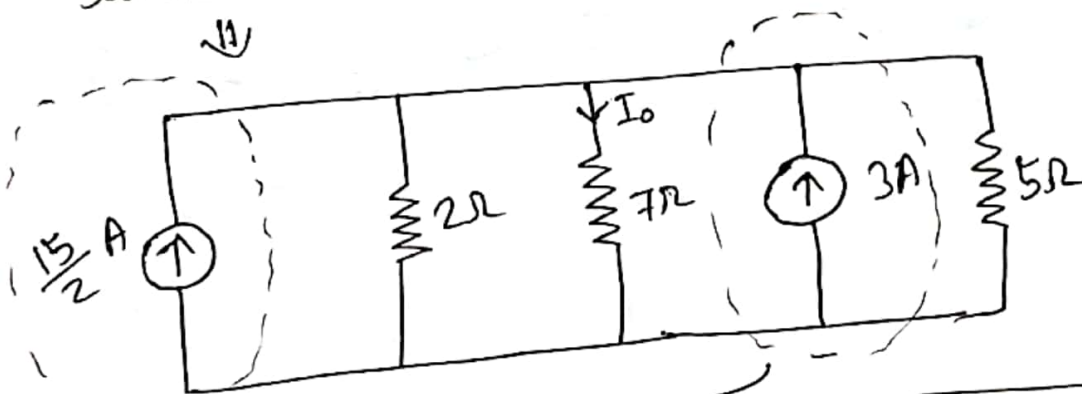

Parallel Current Source
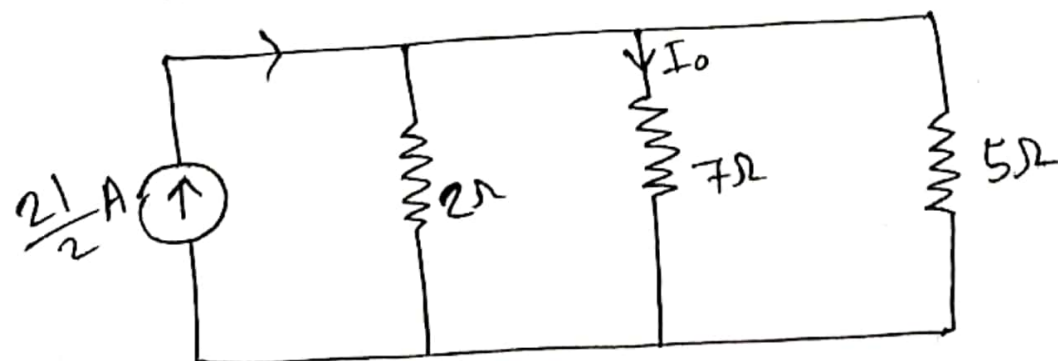
$$I_{eq} = \left(\frac{15}{2} + 3 \right) A = \frac{21}{2} A$$



∴ Now, We can directly apply Current Divider Rule [Lecture 3]

121-1 (at 100 W)

Q. 2

$$\therefore I_0 = I \times \frac{\frac{1}{7}}{\frac{1}{2} + \frac{1}{7} + \frac{1}{5}} \text{ A}$$

$$= \frac{21}{2} \times \frac{\frac{1}{7}}{\frac{1}{2} + \frac{1}{7} + \frac{1}{5}} \text{ A}$$

$$= \boxed{1.78 \text{ A}}$$


(Ans.)




$A \left(\frac{1}{5} + \frac{1}{10} \right)$...

Source Transformation with Dependent Sources


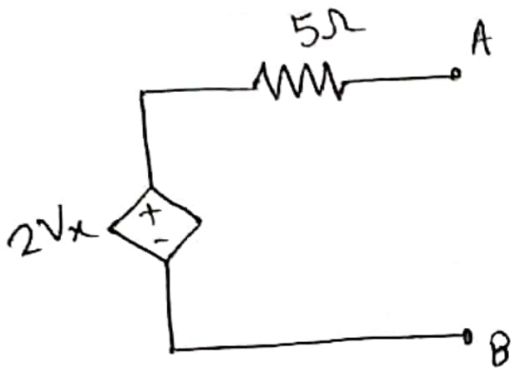
We can do the ST for dependent sources using exactly the same procedure.


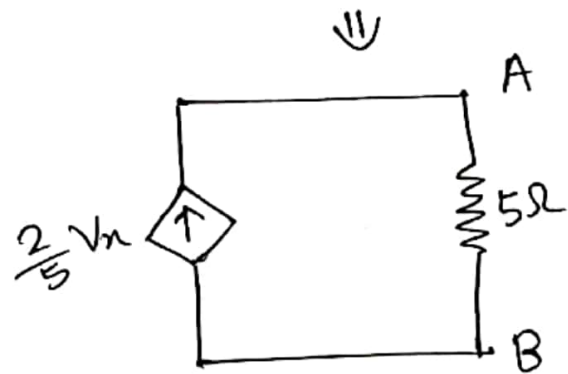
$$\Rightarrow I = \frac{V}{R} = \frac{2V_x}{5} = \frac{2}{5} V_x$$




Similarly,

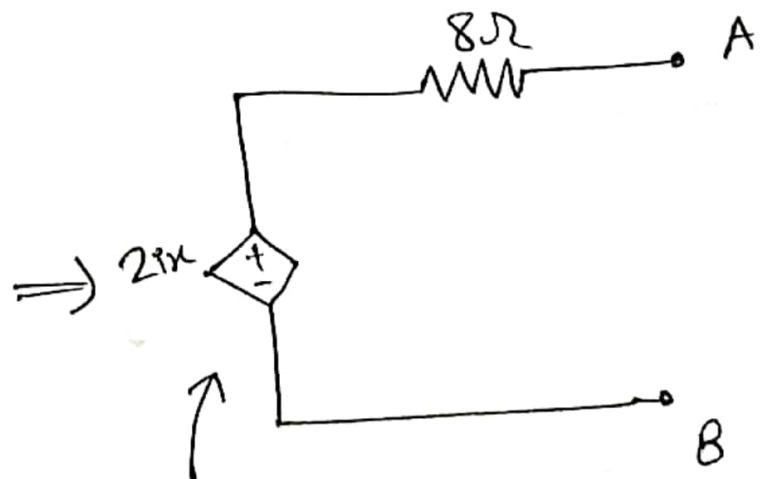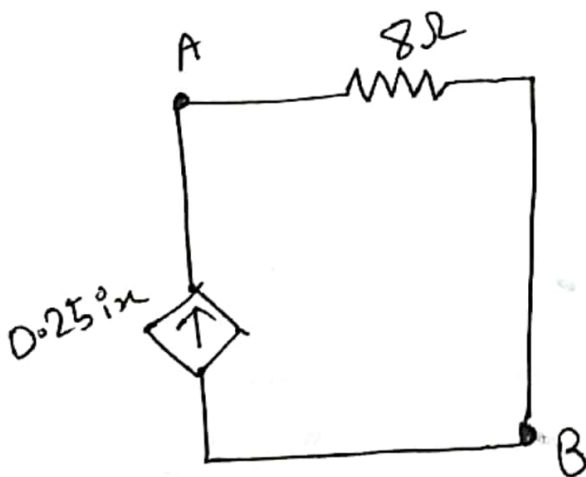


$$V = IR = 0.25i_x \times 8 = 2i_x$$

② Source Tx.

Given,

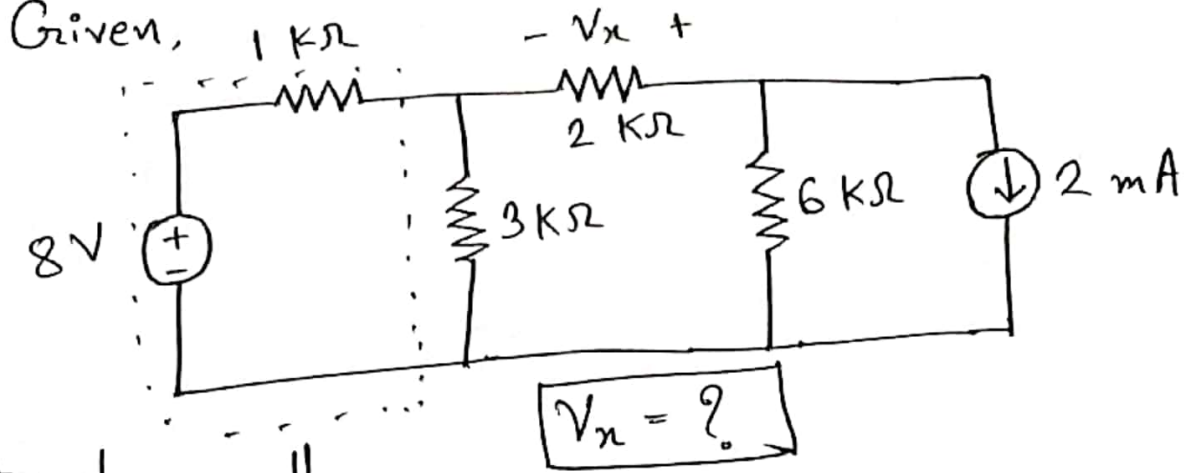


Step-1

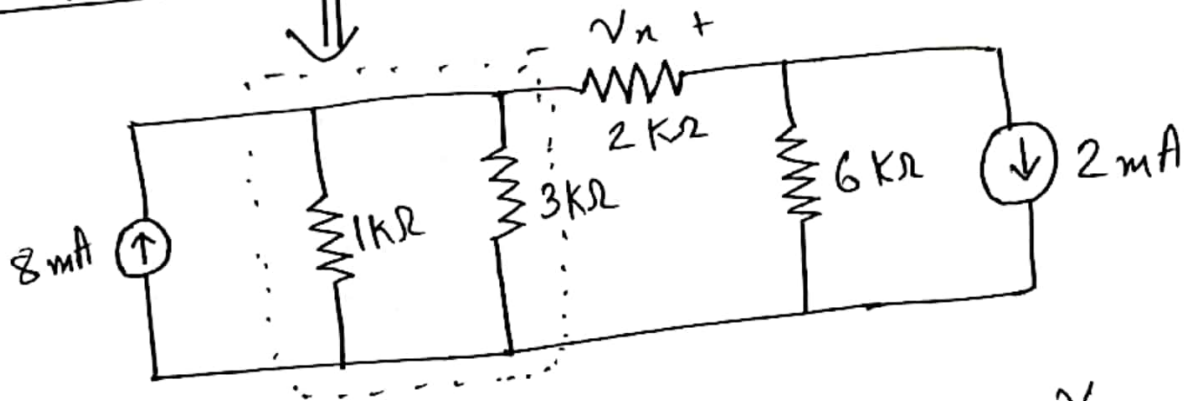


$$\square I = \frac{V}{R} = 8 \text{ mA}$$

Step-2

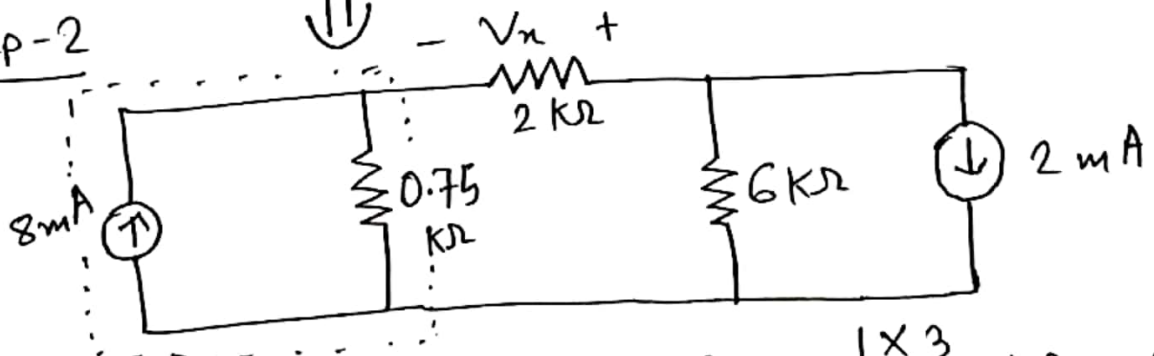


$$\square R_p = \frac{1 \times 3}{1 + 3} \text{ k}\Omega = 0.75 \text{ k}\Omega$$

Step-3

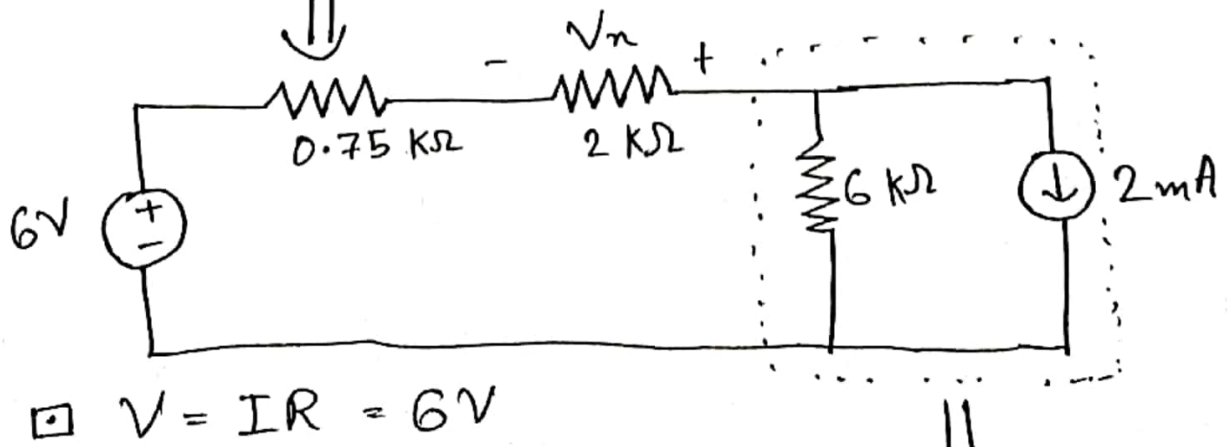

$$\square V = IR = 6 \text{ V}$$

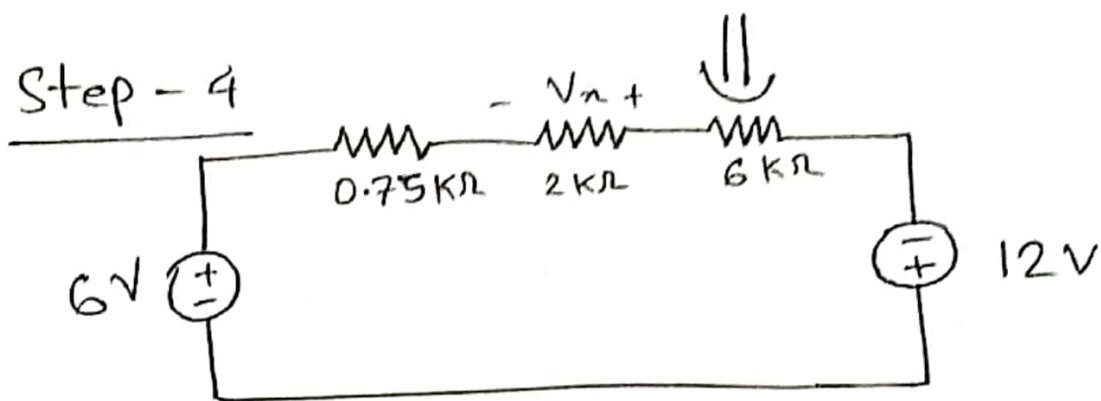


$$\square V = IR = 6 \times 2 = 12 \text{ V}$$

Common Mistake → Wrong Polarity of Voltage Source.

Here, Current source was making current flow downwards. $\downarrow 2 \text{ mA}$ ⇒ So the polarity of Voltage

source will be $\boxed{\downarrow 12 \text{ V}}$ or $\boxed{+ -12 \text{ V}}$. Not $\boxed{\uparrow 12 \text{ V}}$.

Step-5

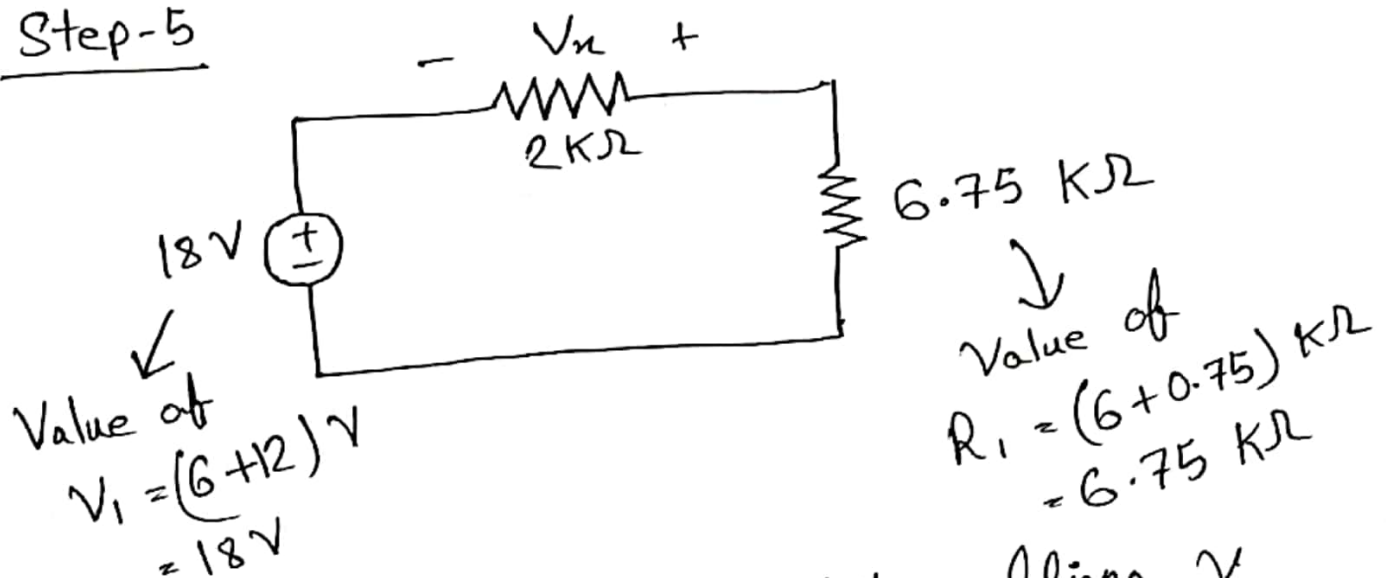

Common Mistake → Mistake while adding V .
With respect to the complete loop, both Voltage sources are of same polarity. So the sum will be $(6 + 12) = 18 \text{ V}$; not 6 V or -6 V .


V_n Calculation

Using Voltage Divider Rule,

$$\begin{aligned} V_n &= - \left(V_1 \times \frac{2}{6.75 + 2} \right) \\ &= - \left(18 \times \frac{2}{8.75} \right) \\ &= \boxed{-4.114 \text{ V}} \end{aligned}$$

Common Mistake:

Wrong Polarity again. Here

V_n is . The negative end is where the high voltage end of source meets.
So, $V_n = (\text{The Voltage drop at } 2\text{K}\Omega \text{ resistance}) \times (-1)$