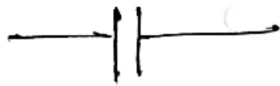



## Week - 8

### Transient Circuit Analysis

#### Capacitors




or,

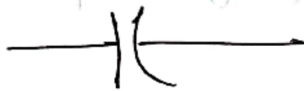

Symbol →

Physical Structure →

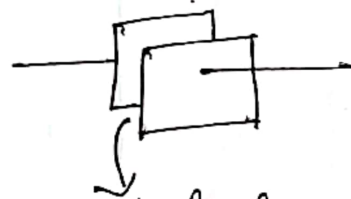

Metal Sheets,

Separated by air or  
some other non-conducting  
material


Basic Property →

Stores Charges  
when voltage is applied across.







Electrical Energy

#### Inductors

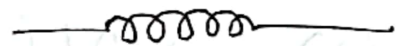


→ Simply a  
coil of wire

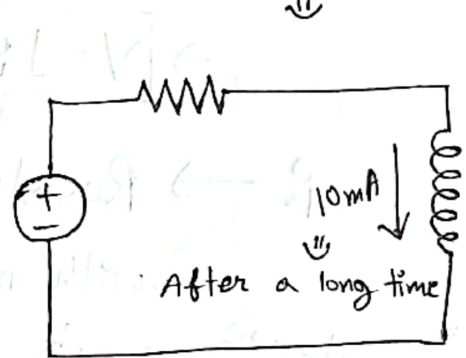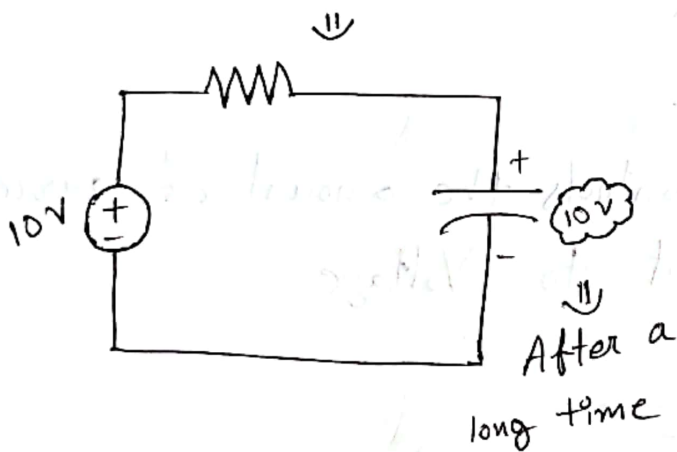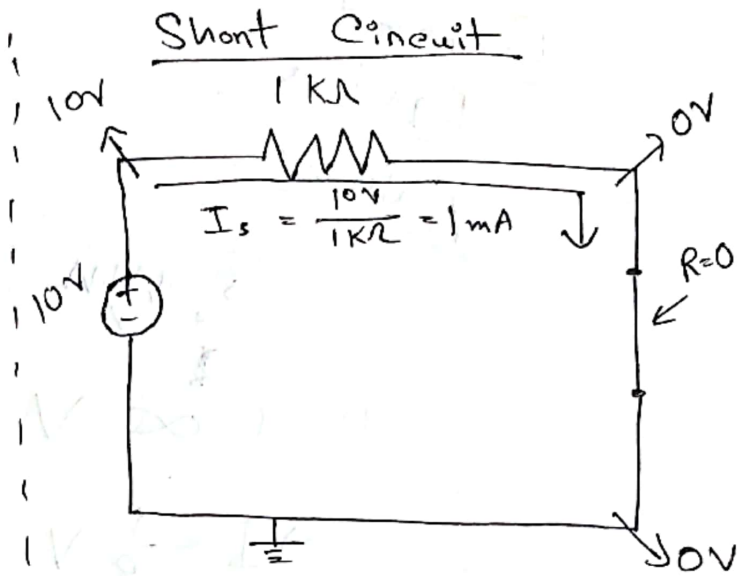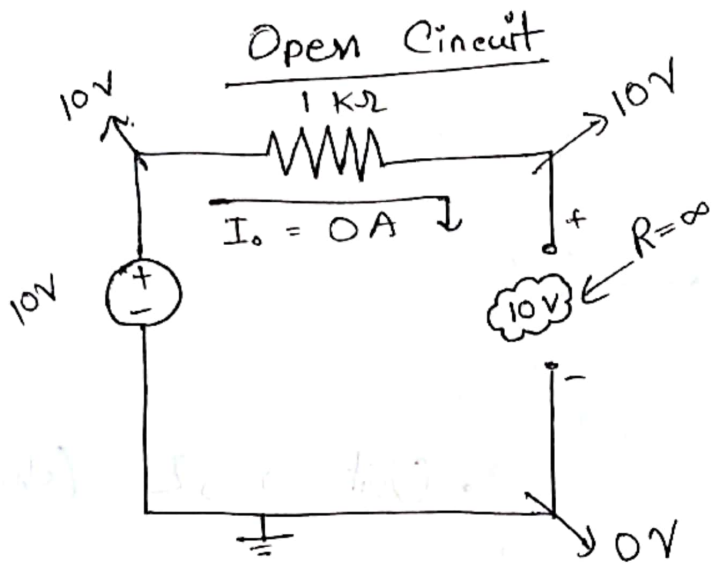
Can store magnetic energy according to Faraday's law.




Eventually acts like a  
Open Circuit

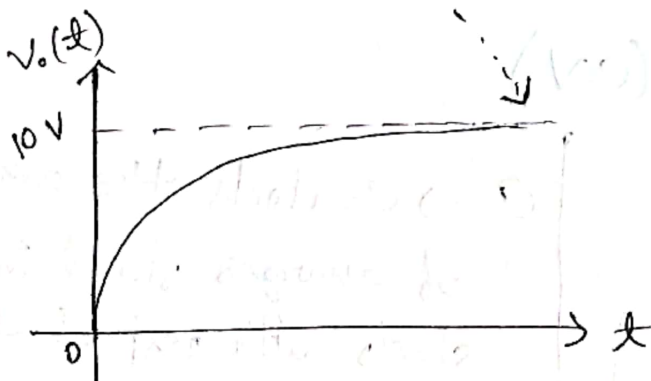

Eventually acts like  
a Shunt circuit.

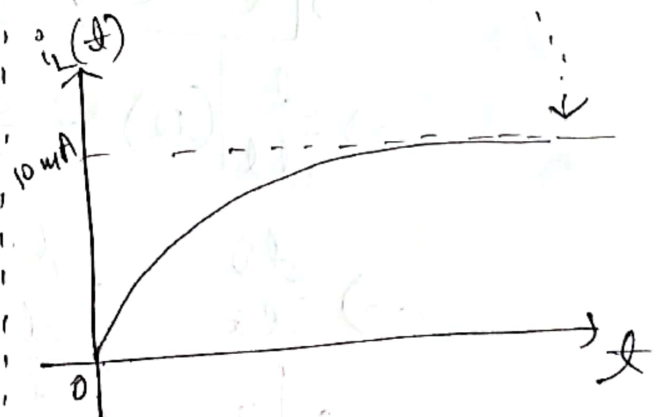

Component  
Equations  
Resistance

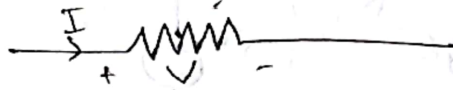

$$I \propto V$$


$$\Rightarrow I = \frac{1}{R} V$$

$$\Rightarrow \boxed{V = IR}$$

• Unit  $\rightarrow \Omega$  (ohm).

$R \rightarrow$  Resists / Controls the amount of current with respect to Voltage.

Capacitance

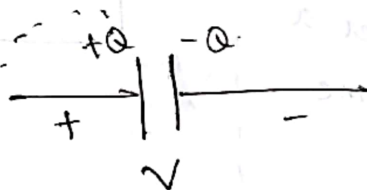

$$Q \propto V$$

$$\Rightarrow \boxed{Q = CV}$$

• Unit  $\rightarrow F$  (Faraday)


$$\Rightarrow \frac{d}{dt}(Q) = \frac{d}{dt}(CV)$$

$$\Rightarrow \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$\Rightarrow \boxed{I = C \frac{dV}{dt}}$$

$C \rightarrow$  Controls the amounts of charges stored in metal sheets with respect to 'Change of Voltage'.

## Inductance

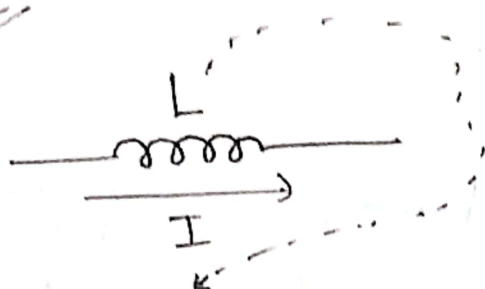

Magnetic Flux

$$\Phi = L I$$


• Unit  $\rightarrow$  H (Henry)

$$\Rightarrow \frac{d\Phi}{dt} = L \frac{dI}{dt}$$

$$\Rightarrow \boxed{V = L \frac{dI}{dt}}$$

$L \rightarrow$  Controls the amount of flux induced with respect to 'Change in Current'.

Why Change for a small time initially?

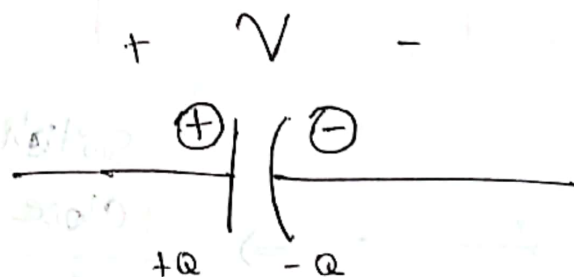


$\Rightarrow$  Voltage applied  $\rightarrow$  Charges start to flow towards the sheets (Creating Current)  $\rightarrow$  A certain amount of charge stored in the sheet  $\rightarrow$  Voltage Difference created, Current flow stopped (almost)  $\rightarrow$  Steady State.

□ Similar in Inductors.
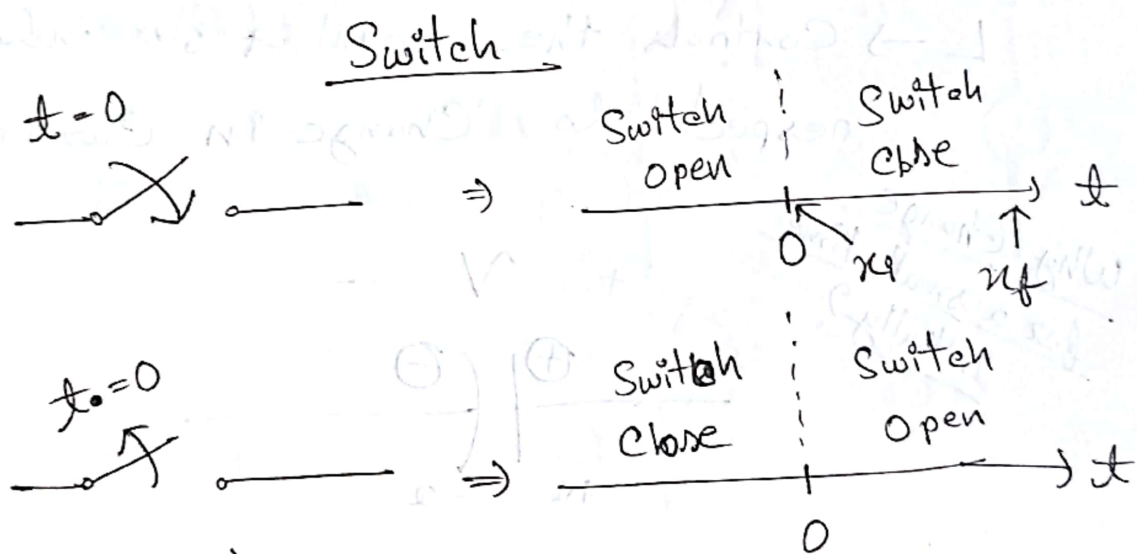
## Transient Analysis

- A function of time.
- There is an initial value and a final (steady state) value.
- After the initial changes, the value doesn't change with time too much anymore.



Basic Formula  
for Exponential Transient Analysis

$$x(t) = x_f + (x_i - x_f) e^{-t/\tau}$$

- $x(t) \rightarrow$  Voltage / current etc.
- $x_i \rightarrow$  Initial value
- $x_f \rightarrow$  final value
- $\tau \rightarrow$  Time constant (sec).




# Time Constant

$\tau$

→ Dictates the rise time etc of the graph.

Capacitor  
 $C$

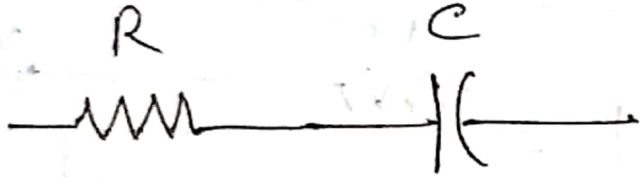

$$\tau = RC$$

• Unit → sec


Inductor  
 $L$



$$\tau = \frac{L}{R}$$

• Unit → sec.

# Capacitance Example

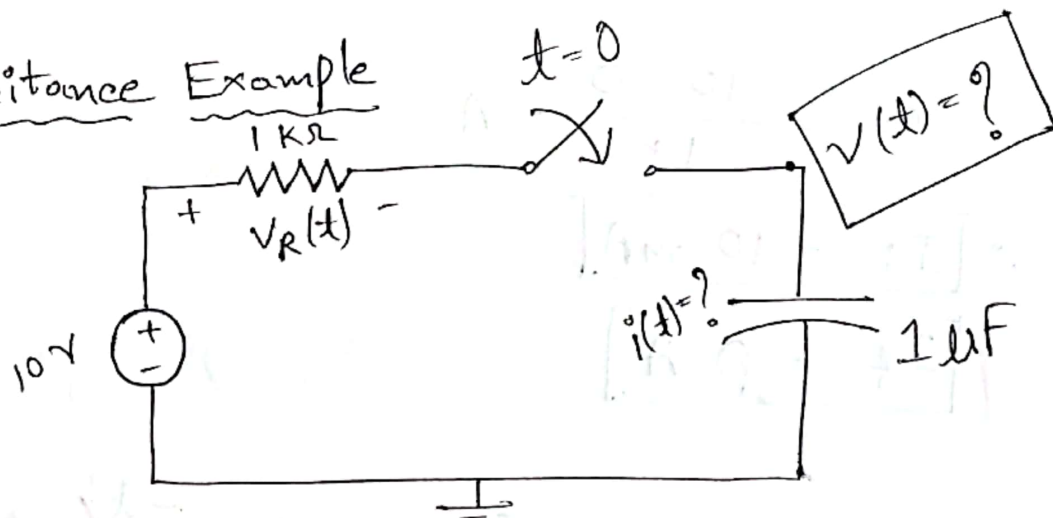


From Basic formula,

$$v(t) = v_f + (v_i - v_f) e^{-t/\tau}$$


$$\tau = RC \text{ [for Capacitor]}$$

$$= 1 \text{ k}\Omega \times 1 \mu\text{F}$$

$$= 10^{-3} \text{ s}$$

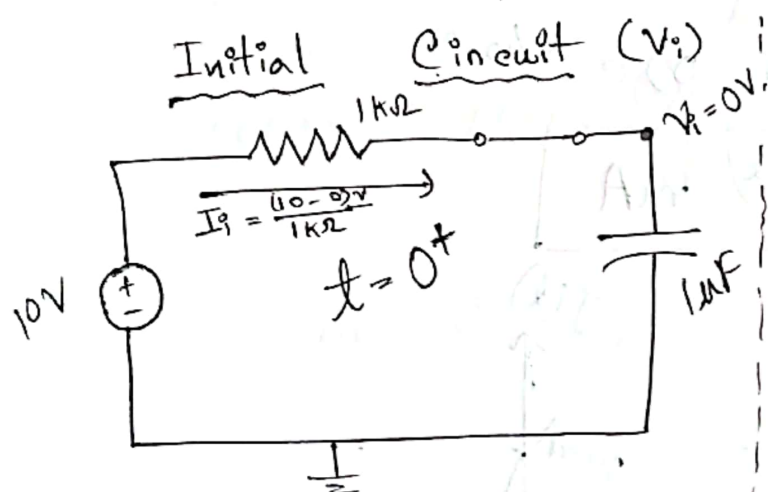

$$v_i = 0 \text{ V}$$

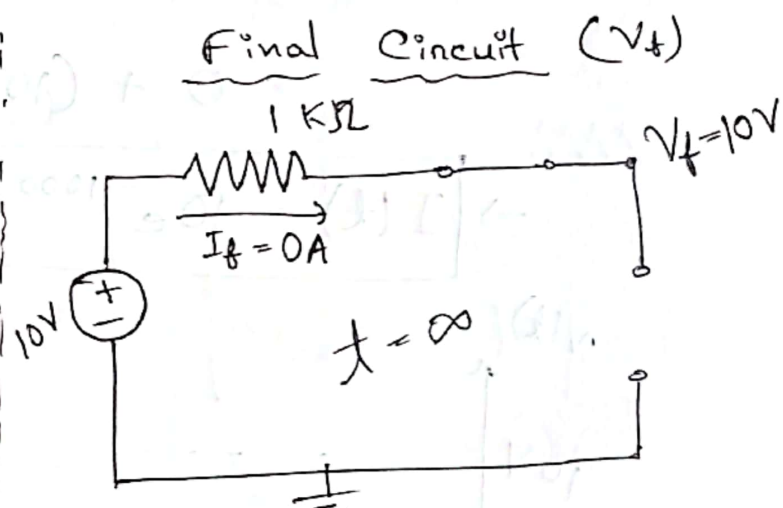

$$v_f = 10 \text{ V}$$

Tip: Think about the graph  
of  $v$  before  $t = 0$

$$I_i = \frac{10 - 0}{1K} A$$

$$\therefore \boxed{I_i = 10 \text{ mA}}$$

$$\boxed{I_f = 0 A}$$

$$\therefore V(t) = V_f + (V_i - V_f) e^{-t/\tau} \quad |\tau = 10^{-3}|$$



$$= 10 + (0 - 10) e^{-1000t} \text{ V}$$

$$\Rightarrow \boxed{V(t) = 10(1 - e^{-1000t}) \text{ V}}$$

$$I(t) = I_f + (I_i - I_f) e^{-t/\tau} \quad |\tau = 10^{-3}|$$


$$= 0 + (10 - 0) e^{-t/10^{-3}}$$
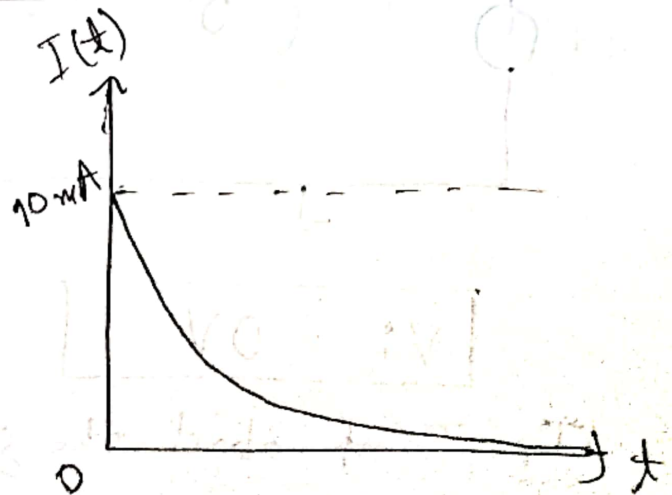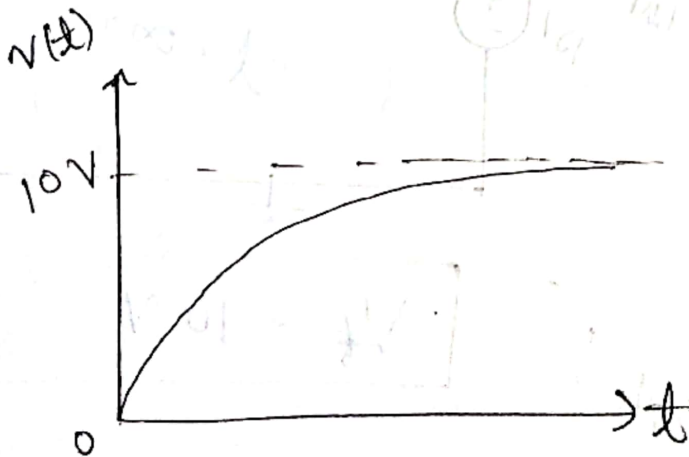
$$\Rightarrow \boxed{I(t) = 10 e^{-1000t} \text{ mA}}$$





## Inductor Example

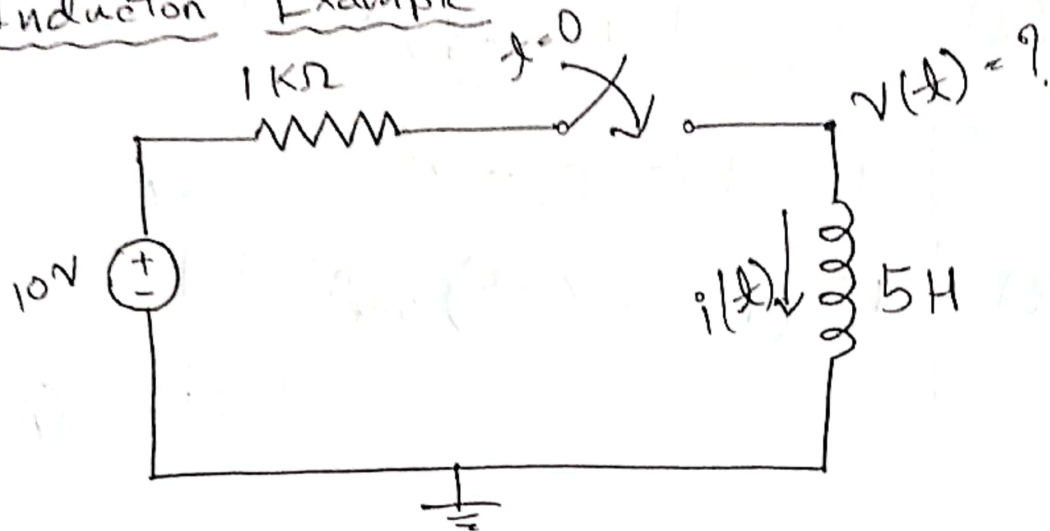


$$\tau = \frac{L}{R}$$

for inductor

$$= \frac{5}{1k}$$


$$= 0.005 \text{ s}$$

Initial Circuit ( $I_i$ )

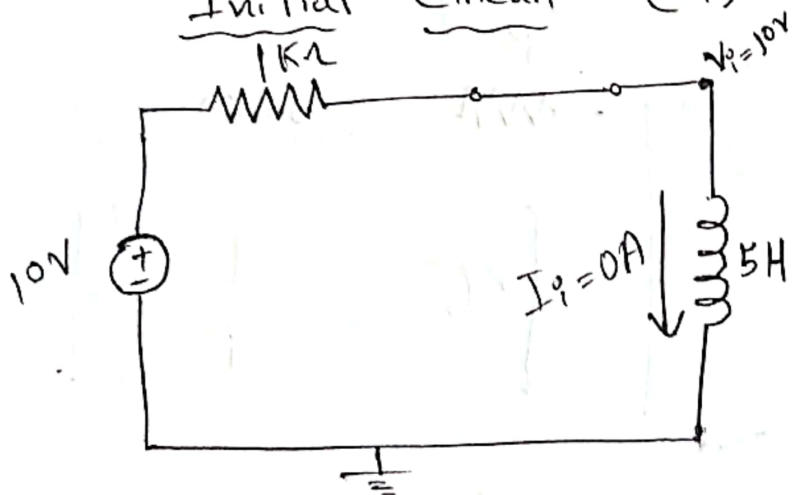

$$I_i = 0A$$

Final Circuit ( $I_f$ )

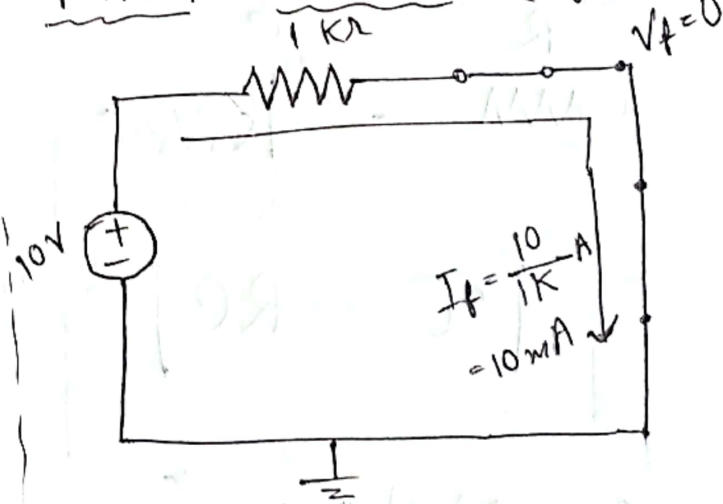

$$I_f = 10 \text{ mA}$$

Tip: Same as before.

$$I(t) = I_f + (I_i - I_f) e^{-t/\tau}$$

$$= 10 + (0 - 10) e^{-t/0.005} \text{ mA}$$

$$\Rightarrow I(t) = 10 (1 - e^{-200t}) \text{ mA}$$

(Ans.)