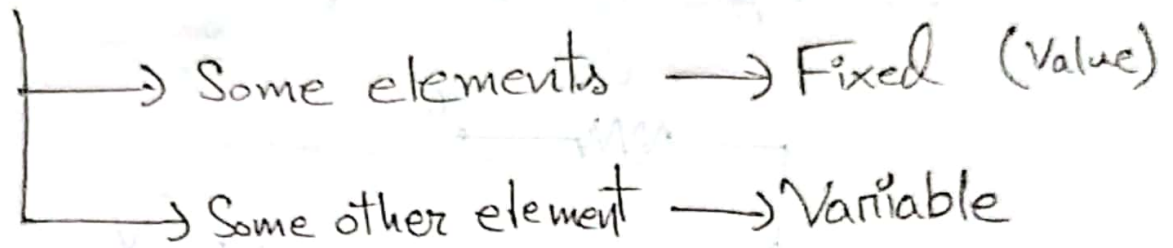


Lecture 10: Circuit Theorems

Thevenin's Theorem

Load


Often within a circuit



That variable element (often consists of resistors/ inductors/capacitors etc) is called **Load**.

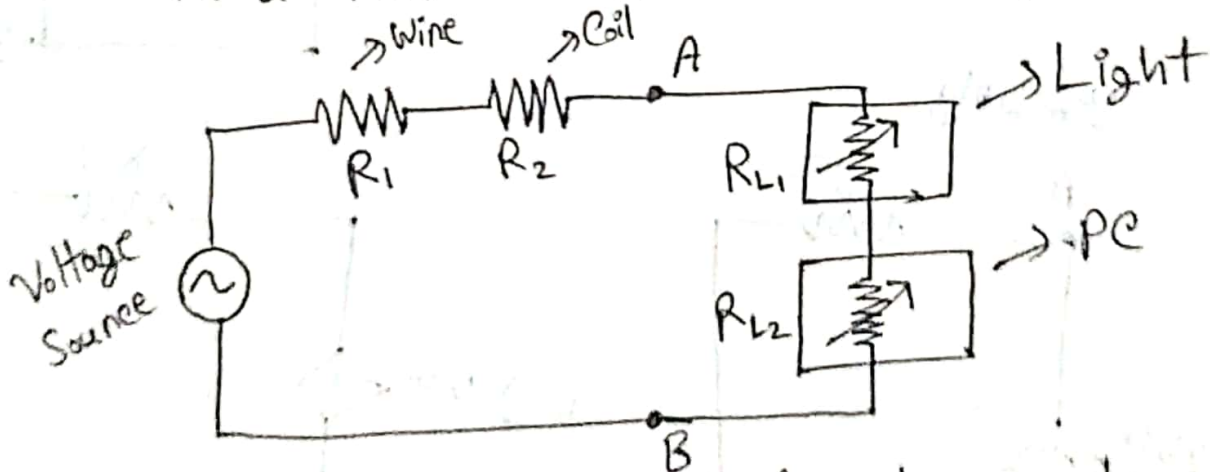
example:

In a Household outlet circuit (simplified)




Here, the A-B terminal denotes a household outlet terminal. The wire resistance R_1 , coil resistance R_2 are **fixed**. But household related resistances (Light R_{L1} , PC R_{L2}) are **variable**.

→ They are variable because they can be changed due to switching on/off, unlike wire resistances. → They are **Loads**.


• Symbol of variable Resistor → 

Circuit Equivalence

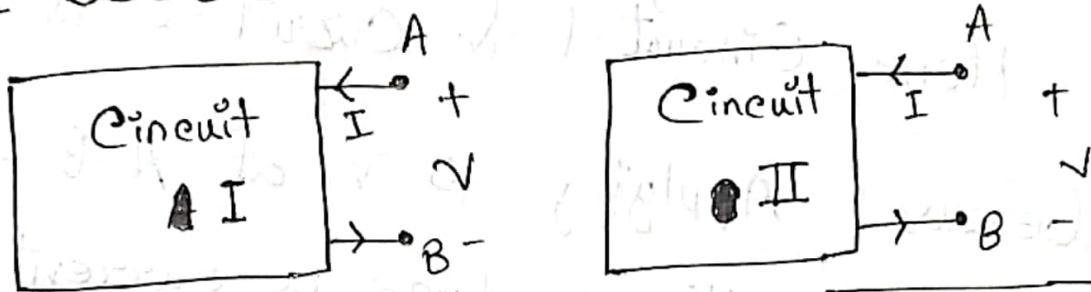


Circuit - I & Circuit - II are **Equivalent** if they have the same Current voltage relationship at their terminals (A-B). That means, If we apply V voltage difference across the A-B terminals, the same current I will flow from A and come out through B (and Vice-versa).

Example

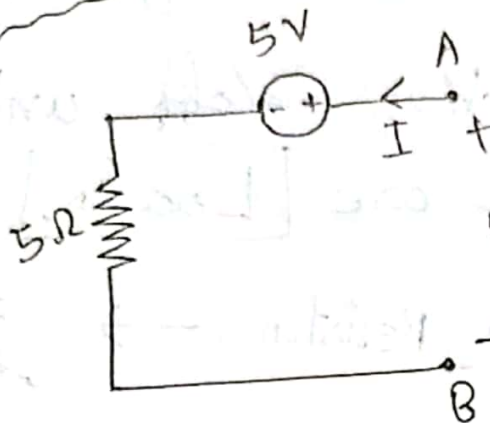


Circuit-1

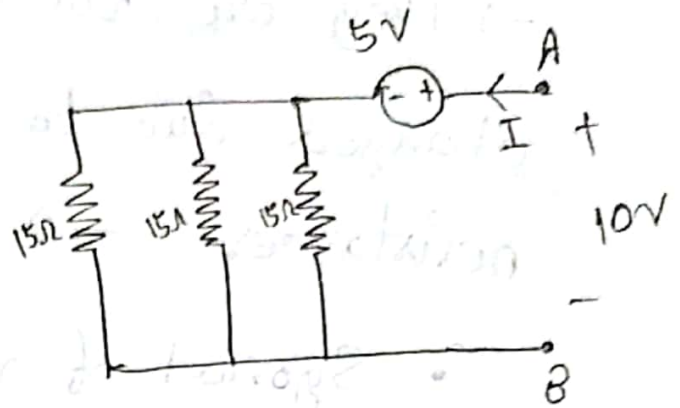


Circuit-2

Hence, Circuit-1 & Circuit-2 is equivalent because: Applying 10 V at A-B terminal, both circuits produce a current $I = 1A$ (same for both) flowing from A.

Linear Two-Terminal Circuit

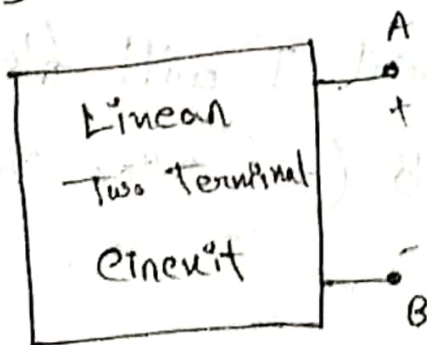


Example

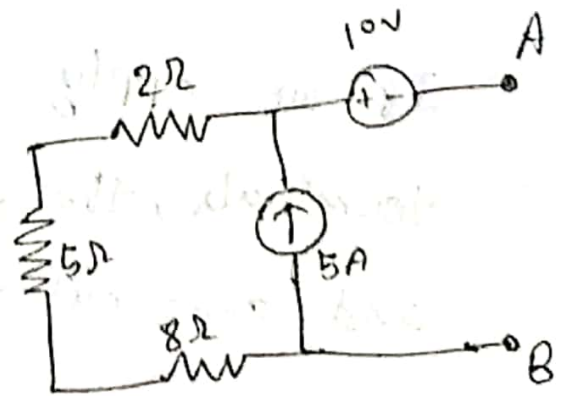

This can be very complex.

Thevenin's Theorem

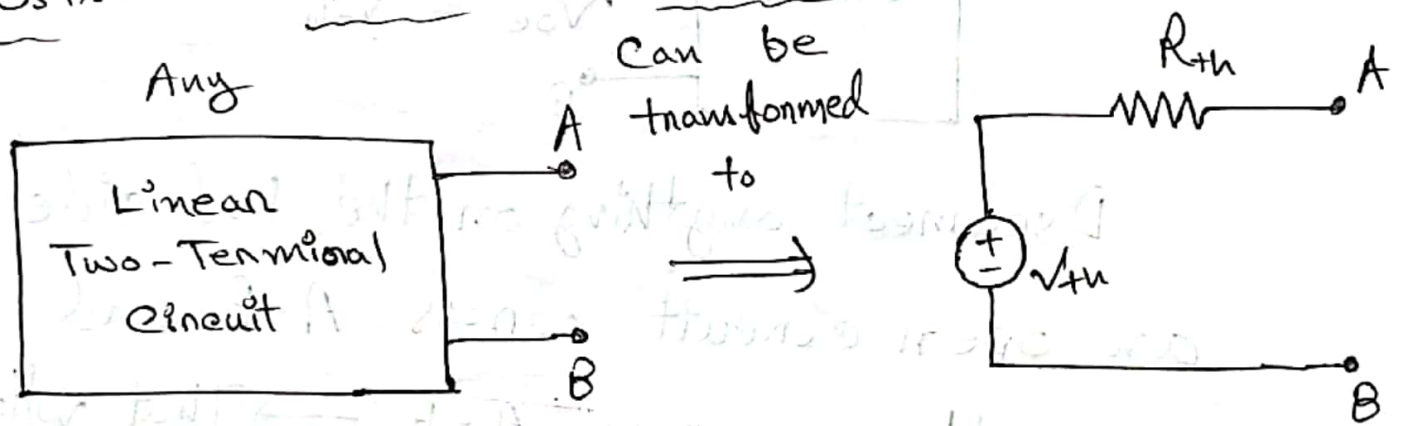"A Linear Two-terminal circuit can be replaced by an Equivalent circuit consisting of a voltage source V_{th} in series with a resistor R_{th} ." [Sadiku 5th Edition page 139]




Can be used to replace the fixed part (often very complex) of a circuit by an equivalent simple circuit.



How to Calculate V_{th} , R_{th}

Step-1

Find V_{oc} across the terminals.

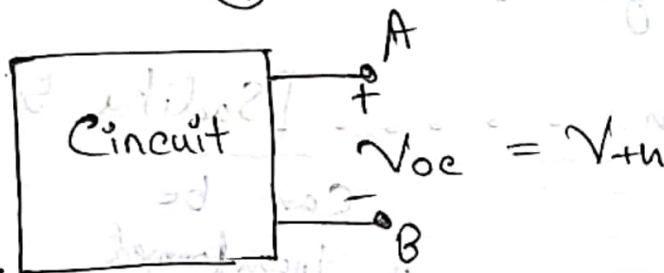


Disconnect anything on the load side to make an open circuit across A-B and calculate the voltage across A-B \rightarrow That voltage = V_{oc}

$$V_{oc} = V_{th}$$

Step-2

Find I_{sc} through the terminals.

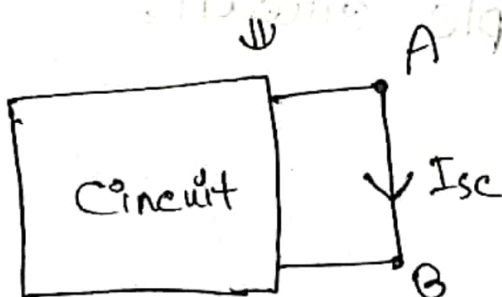

Ignore all other elements on the load side to ~~ma~~ short A & B terminal and calculate the current flowing from A to B. \rightarrow That current = I_{sc} .


Step-3

Find R_{th} .


$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

Step-4

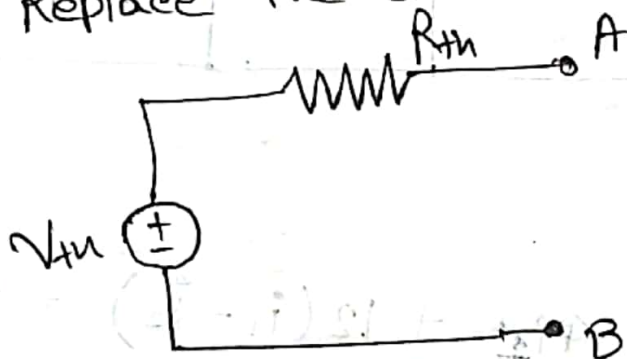
Replace the circuit with the Thevenin Equivalent circuit.



Example-14.8

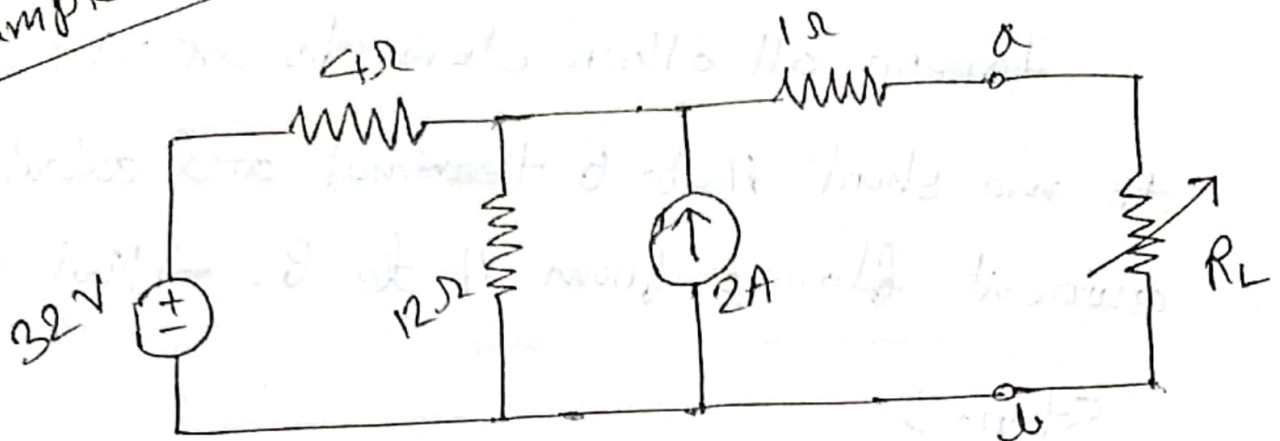

Step-1

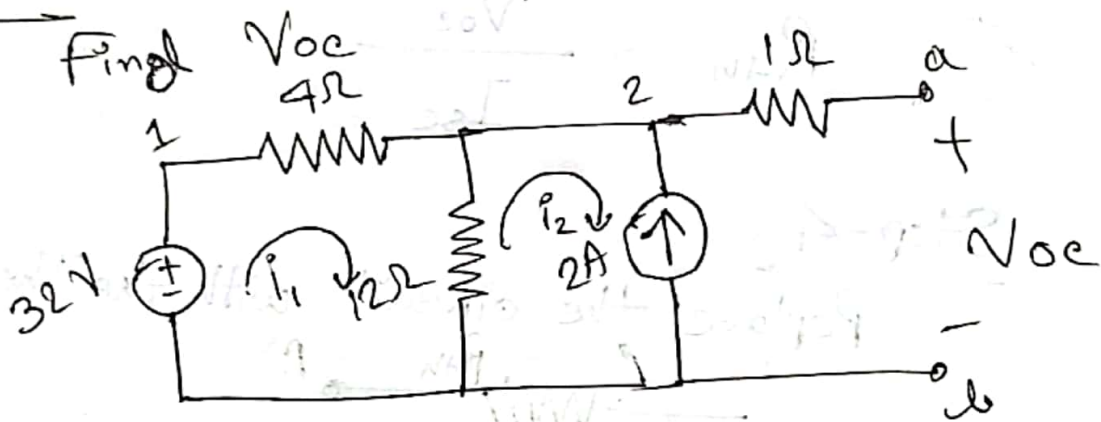

Loop-1

$$-32 + 4i_1 + 12(i_1 - i_2) = 0$$

$$\Rightarrow 16i_1 - 12i_2 = 32 \quad \text{--- (i)}$$

Loop-2

$$i_2 = -2 \quad \text{--- (ii)}$$

$$\therefore \text{Solving (i), (ii)} \rightarrow \begin{aligned} i_1 &= 0.5 \text{ A} \\ i_2 &= -2 \text{ A} \end{aligned}$$


$$\therefore V_{Th} = V_2 = 12(i_1 - i_2) = 12(0.5 + 2) \text{ V}$$

$$= 30 \text{ V}$$

$$\therefore V_{th} = 30 \text{ V}$$

Step-2

Find I_{sc}

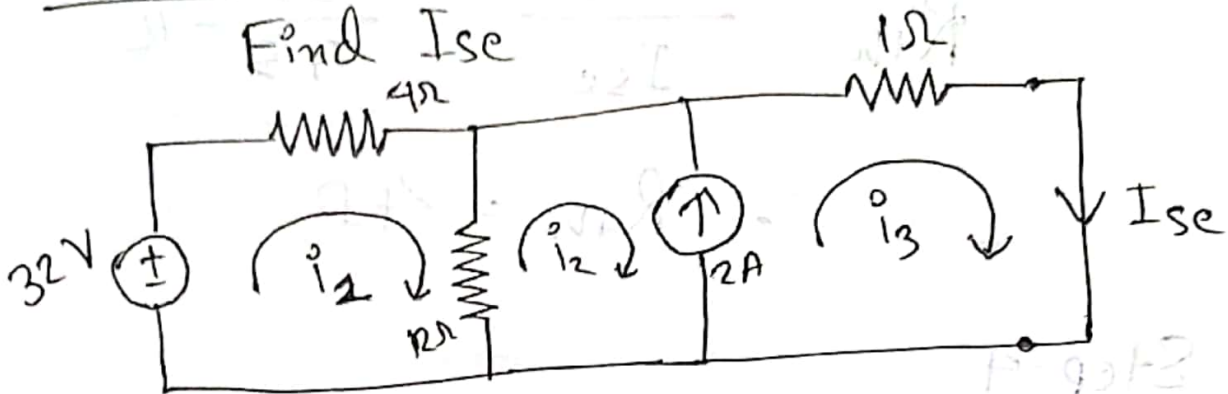

Loop-1

$$16i_1 - 12i_2 = 32 \quad \text{--- (i)}$$

Loop-2 & 3 (Supermesh)

$$i_3 - i_2 = 2 \quad \text{--- (ii)}$$

$$12(i_2 - i_1) + i_3 = 0$$

$$\Rightarrow -12i_1 + 12i_2 + i_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii), (iii),

$$i_1 = 6.125 \text{ A}$$

$$i_2 = 5.5 \text{ A}$$

$$i_3 = 7.5 \text{ A}$$

$$\therefore I_{sc} = i_3 = 7.5 \text{ A}$$

Step-3


Find R_{th} ,

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{30}{7.5} \Omega$$

$$\therefore R_{th} = 4 \Omega$$

Step-4

Construct the simplified circuit,

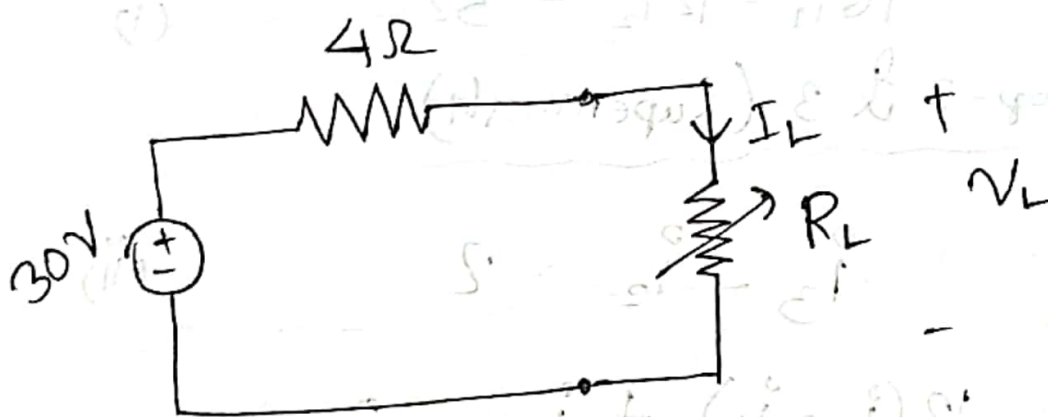

$$V_L = ?$$

$$I_L = ?$$

$R_L = 6 \Omega \rightarrow$ Using Voltage Divider Rule,

$$V_L = 30 \times \frac{6}{4+6} = \boxed{18V}$$

$$I_L = \frac{\Delta V}{R_{eq}} = \frac{30}{4+6} = \boxed{3A}$$

$$R_L = 16 \Omega \rightarrow I_L = \frac{30}{4+16} = \boxed{1.5A}$$

$$R_L = 36 \Omega \rightarrow I_L = \frac{30}{4+36} = \boxed{0.75A}$$

(Ans.)

An Alternative way to calculate R_{th}

This method is only applicable when

there is no dependent source in the circuit.

V_{th} & R_{th} Calculation

Step-1

Same as before.

Step-2

SKIP

Step-3


a)

Replace all voltage sources with short



b)

Replace all current sources with open

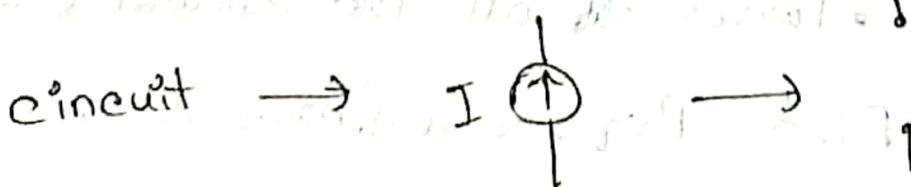

c) Find the Equivalent Resistance R_{eq} seeing from a-b terminal.

Step-4 \rightarrow same as before.

The previous problem


Step - 1

Same as before


Step - 2

SKIP

Step - 3

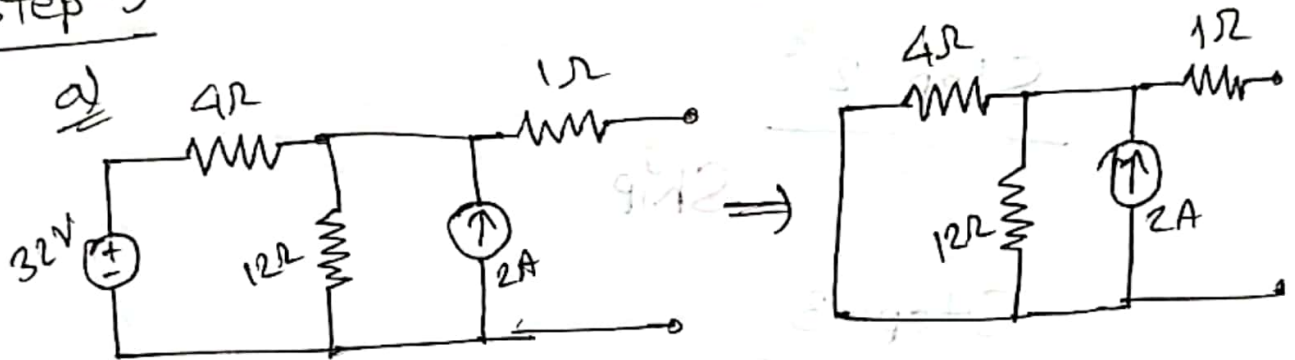



• Turned off all the voltage sources

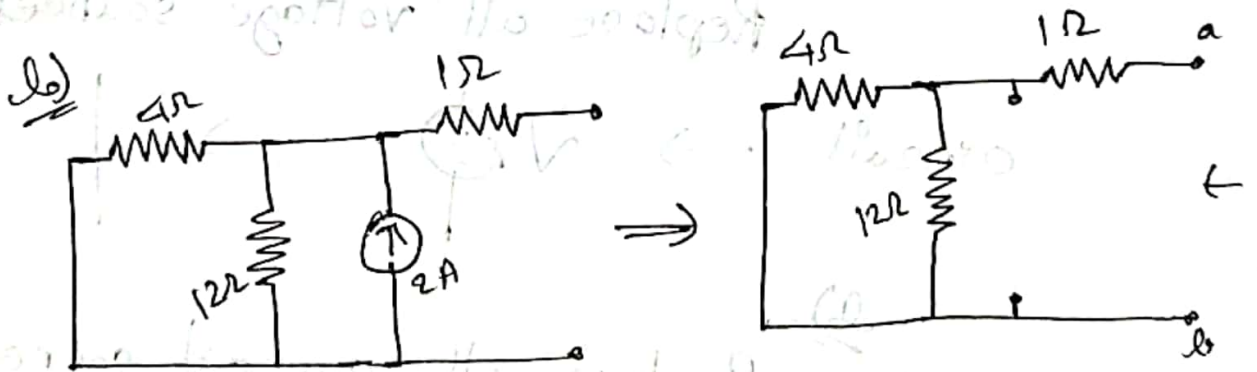

• Turned off all the current sources

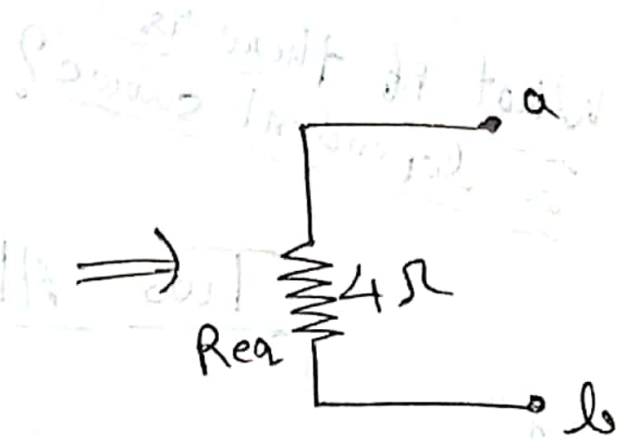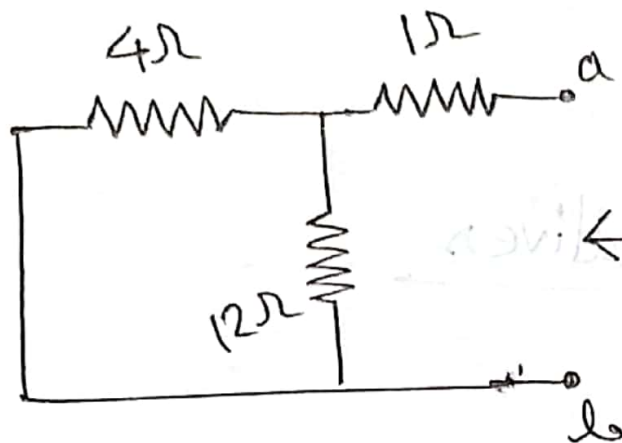2) Find R_{eq} seen from a-b.

$$\begin{aligned} R_{eq} &= 1 + 4 \parallel 12 \\ &= 1 + \left(\frac{1}{4} + \frac{1}{12} \right)^{-1} \Omega = \boxed{4\Omega} \end{aligned}$$



$$R_{th} = R_{eq} = 4\Omega$$

Step-4

Same as before.

What if there is
a dependent source?

Two Alternatives

1 Use the first approach

$$V_{th} \rightarrow I_{sc} \rightarrow R_{th} = \frac{V_{th}}{I_{sc}}$$

Simply using Mesh Analysis everytime.
/Nodal
/ST

2 Use the second approach using a
dummy voltage source
⇓


a) Between a-b \rightarrow place a 1V voltage source

b) Turn all other independent sources off
while keeping the dependent sources intact.

c) Analyse the circuit to find out the current
 i_o flowing through a.

$$R_{th} = 1/i_o$$

Example

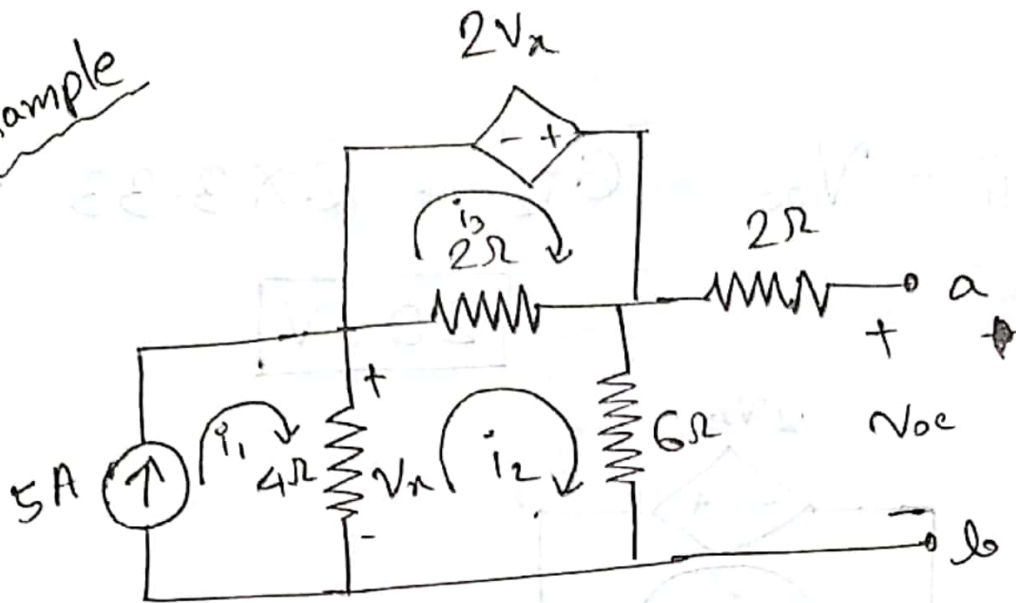

Step-1

$$V_n = 4(i_1 - i_2)$$

Loop-1

$$i_1 = 5 \quad (i)$$

Loop-2

$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$$

$$\Rightarrow -4i_1 + 12i_2 - 2i_3 = 0 \quad (ii)$$

Loop-3

$$2(i_3 - i_2) - 2V_n = 0$$

$$\Rightarrow 2i_3 - 2i_2 - 2 \cdot 4(i_1 - i_2) = 0$$

$$\Rightarrow -8i_1 + 6i_2 + 2i_3 = 0 \quad (iii)$$


Solving i, ii, iii,

$$i_1 = 5 \text{ A}, \quad i_2 = 3.33 \text{ A}, \quad i_3 = 10 \text{ A}.$$

$$V_{th} = V_{oc} = 6i_2 = 6 \times 3.33 \text{ V}$$

$$= \boxed{2.0 \text{ V.}}$$

Step-2
 R_{th}

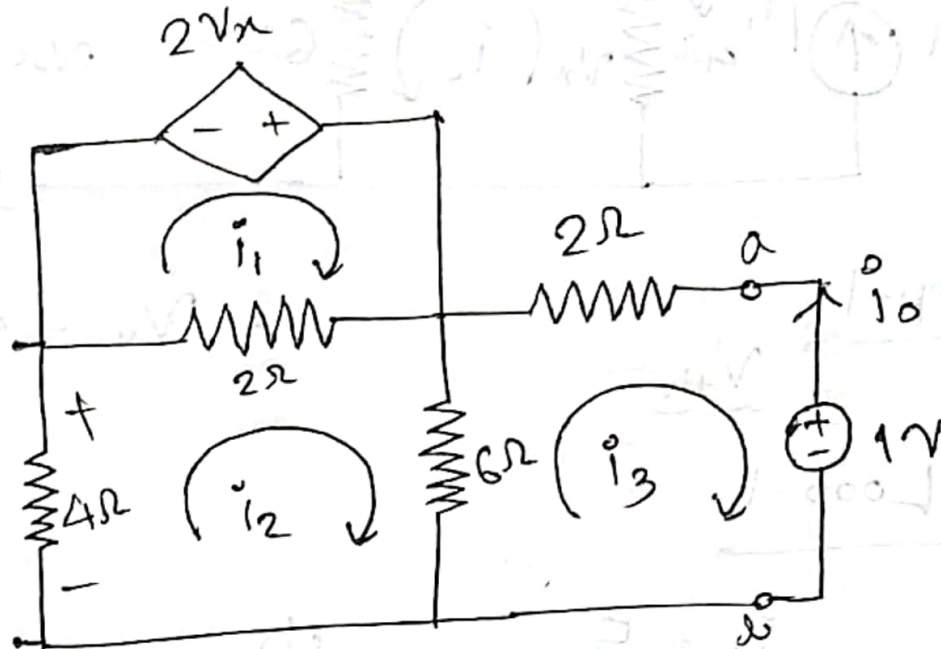

Loop-1

$$2(i_1 - i_2) - 2V_x = 0$$

$$\Rightarrow 2i_1 - 2i_2 - 2(-4i_2) = 0$$

$$\Rightarrow 2i_1 + 6i_2 = 0 \quad \text{--- (i)}$$

Loop-2

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$

$$\Rightarrow -2i_1 + 12i_2 - 6i_3 = 0 \quad \text{--- (ii)}$$

Loop-3

$$6(i_3 - i_2) + 2i_3 + 1 = 0$$

$$\Rightarrow -6i_2 + 8i_3 = -1 \quad \text{--- (iii)}$$


Solving for $i_1, i_2, i_3,$

$$i_3 = -0.1667 \text{ A}$$

Hence, $i_o = -i_3$


$$\therefore i_o = 0.1667 \text{ A}$$
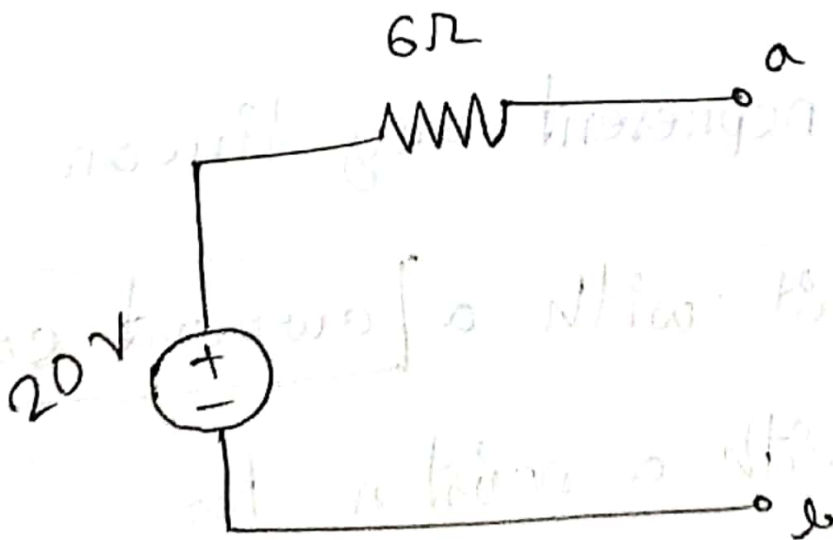
$$\therefore R_{th} = \frac{1}{i_o} = \boxed{6 \Omega}$$



Thevenin Equivalent Circuit.

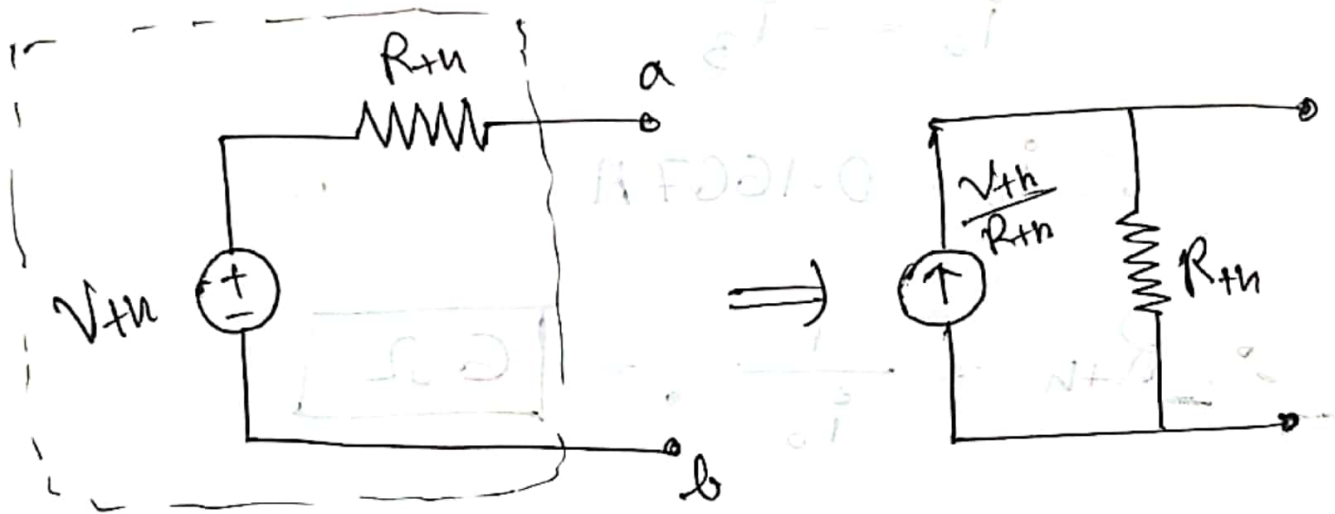
Applying
Source Transformation
to a Thevenin Eq.
to a Circuit



∴ We can represent any linear two terminal circuit with a current source in parallel with a resistor too.

Norton's Theorem

Sadiker 5th Edi. → Page 145.

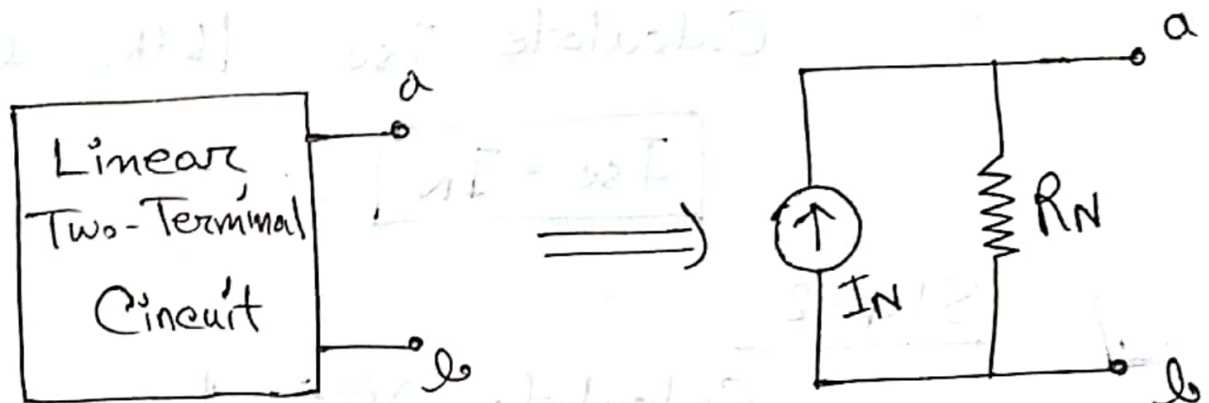

Relationships
with Thevenin
Circuit

$$1. R_N = R_{th}$$
$$2. I_N = \frac{V_{th}}{R_{th}}$$

$I_N = I_{sc}$ | The I_{sc} we calculated in step-2 of Thevenin |

How to Calculate I_N , R_N

Step-1

Calculate I_{sc} | Like before |

$$I_{sc} = I_N$$

Step-2

Calculate V_{oc}

Step-3

Find R_N

$$R_N = \frac{V_{oc}}{I_{sc}}$$

Step-4




Norton Equivalent Circuit


Alternative ways

$R_N = R_{th}$. \therefore Everything else exactly the same as Thevenin.


Example

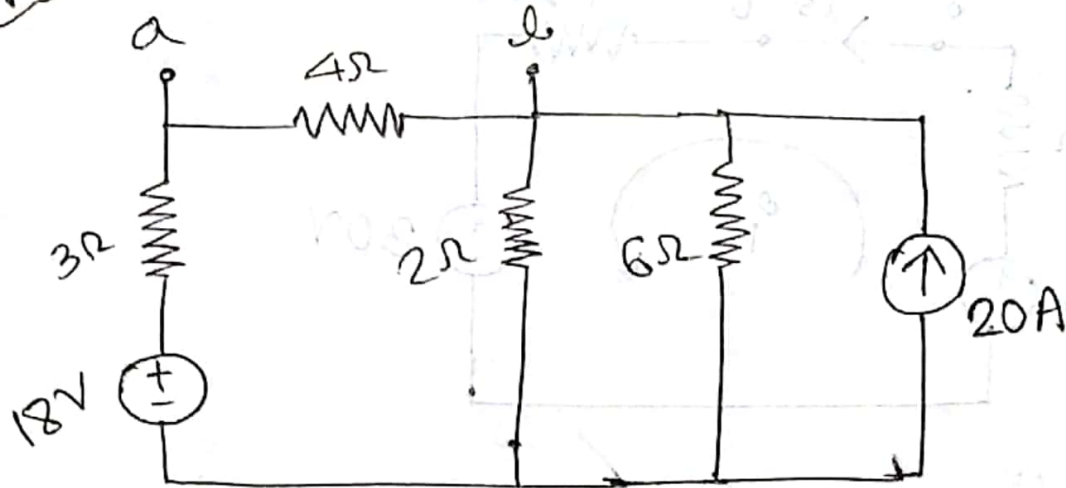


Step-1

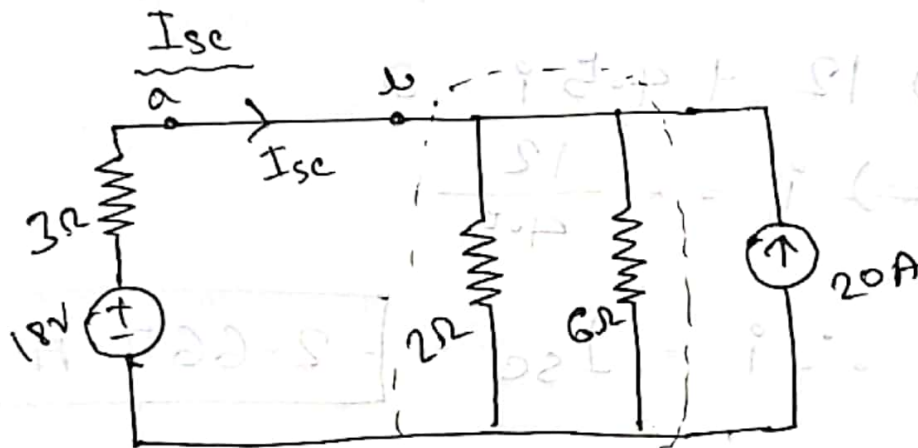
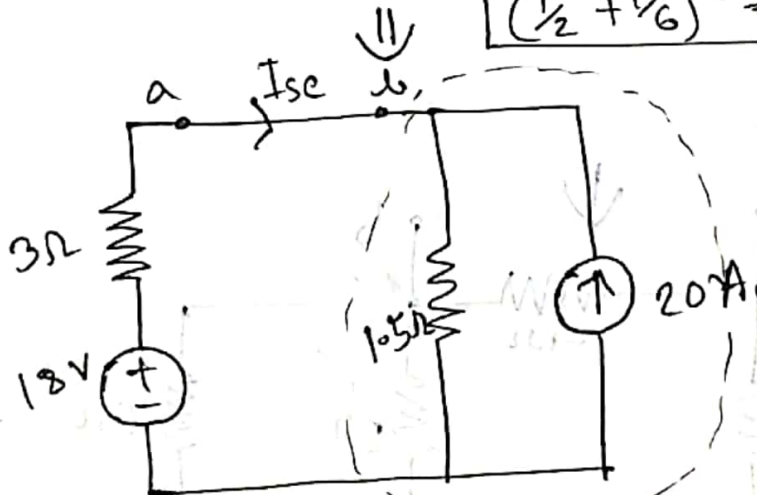
$$\left(\frac{1}{2} + \frac{1}{6}\right)^{-1} = 1.5 \quad \leftarrow R_{eq}$$



$$V_{th} = 20 \times 1.5 = 30V$$

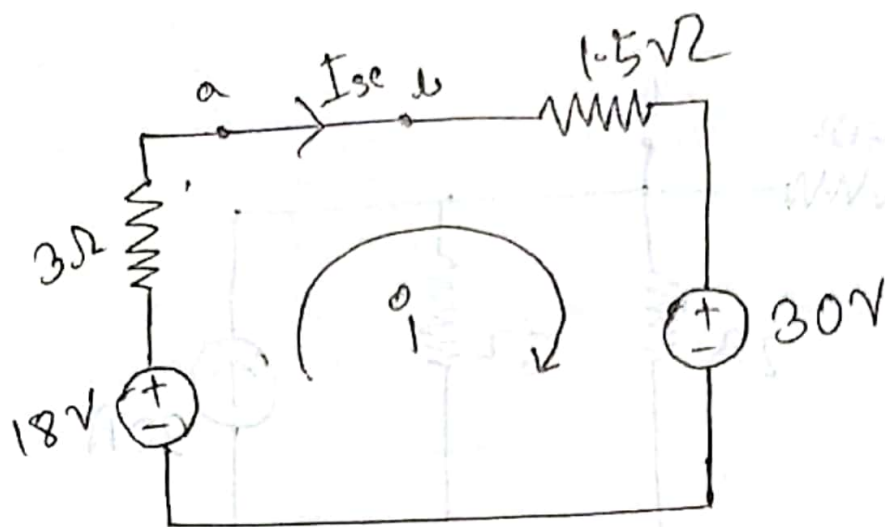

$$\therefore -18 + 3i + 1.5i + 30 = 0$$


$$\Rightarrow 12 + 4.5i = 0$$

$$\Rightarrow i = -\frac{12}{4.5}$$

$$\therefore i = I_{sc} = \boxed{-2.667 \text{ A}}$$

Step-2

R_{th}

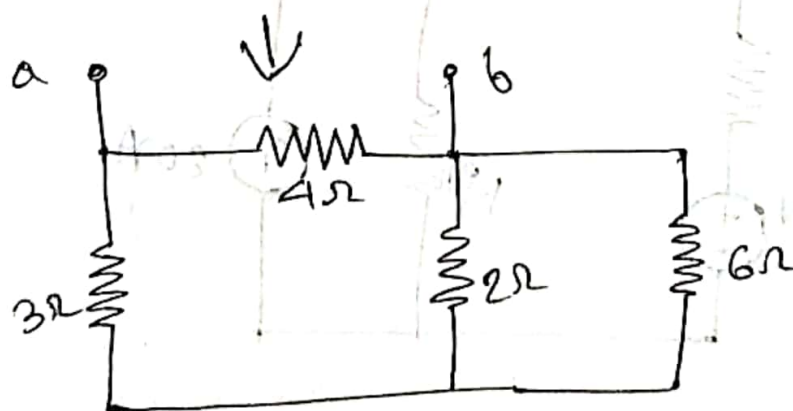

18V voltage source shorted, 20A current source open circuit

$$R_{eq} = (3 + 2 \parallel 6) \parallel 4$$

$\left\{ \begin{array}{l} 2\Omega \text{ \& } 6\Omega \text{ in parallel, they are in series with } 3\Omega \\ \text{All others in parallel with } 4\Omega \end{array} \right.$

$$= (3 \parallel (\frac{1}{2} + \frac{1}{6})^{-1}) \parallel 4$$

$$= (3 + 1.5) \parallel 4$$

$$= 4.5 \parallel 4$$

$$= (\frac{1}{4.5} + \frac{1}{4})^{-1}$$

$$= 2.12 \Omega$$

$$\therefore R_{eq} = R_N = 2.12 \Omega$$

Norton Equivalent Circuit

