
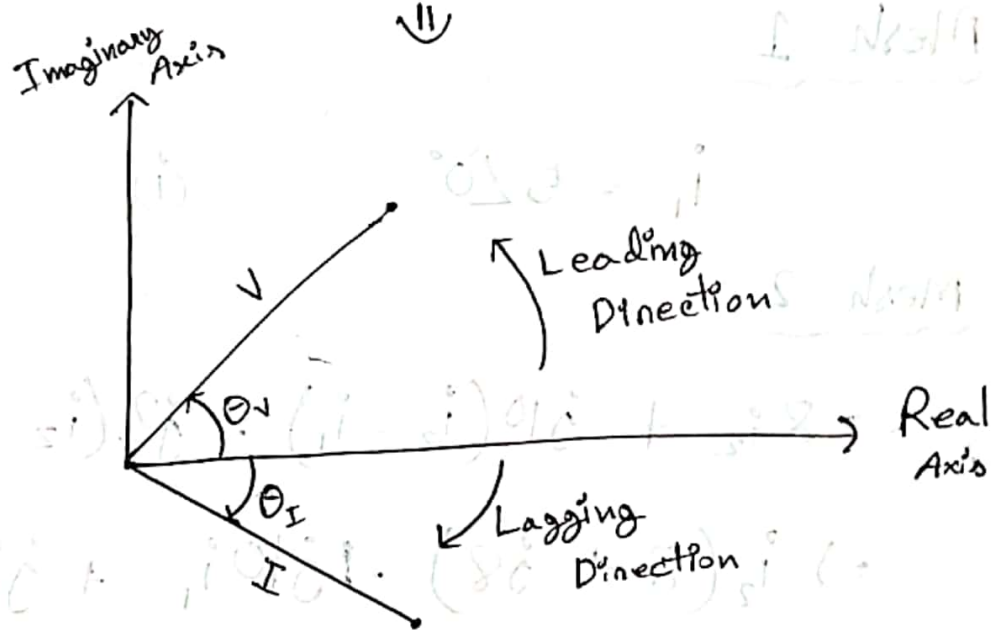


# Lecture 16 AC Power

## Phasor Diagram

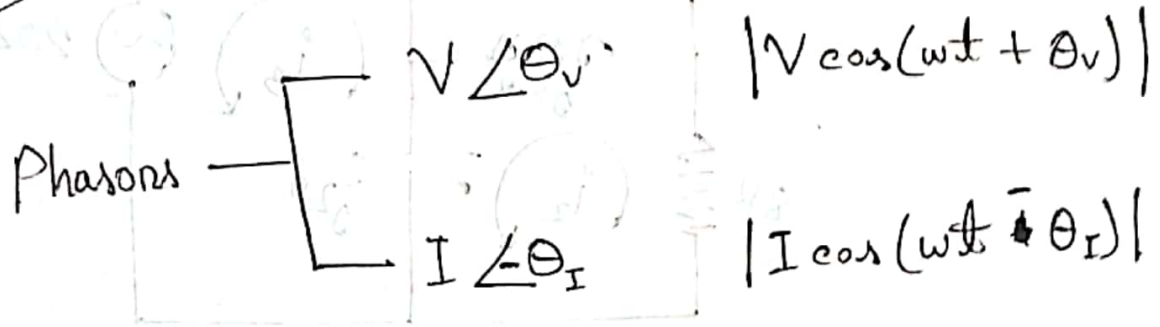


Representing a phasor in a Real-Imaginary  
 → Complex plane. Such representations are  
 called Phasor Diagrams.

□ Here, Voltage is leading current by  $\theta_V + \theta_I$  degrees/radians.

## AC Power


### Instantaneous Power

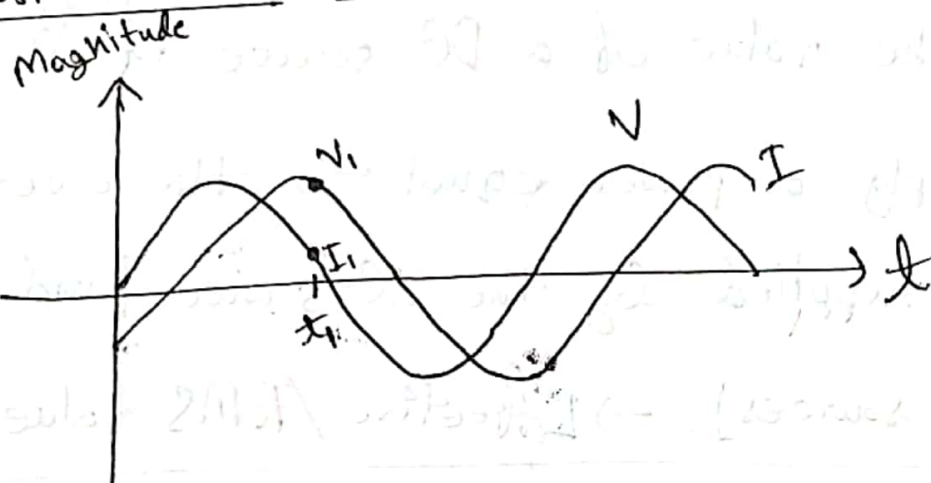

At  $[t_1]$  time instant  $\rightarrow$  Instantaneous Power =  $\boxed{V_1 I_1}$

□ In DC, Instantaneous Power  $\Rightarrow$  Constant.

### Average Power

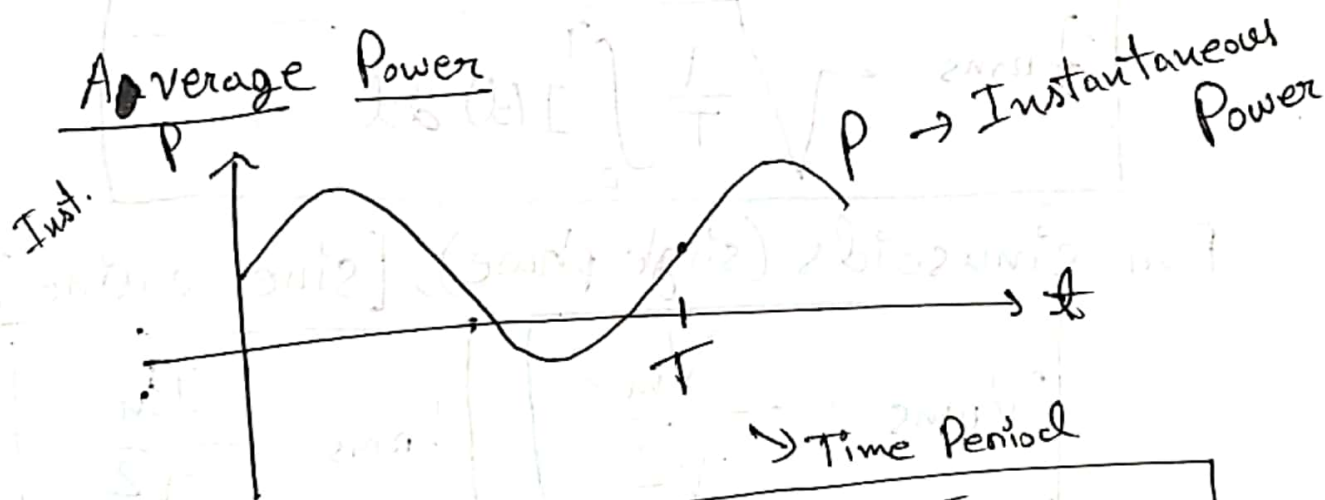

Average Power, 
$$P_{avg} = \frac{1}{T} \int_0^T P dt$$

$\downarrow$   
The Power across a time period divided by the time period  $\rightarrow$  <sup>Inst.</sup>Power per unit time.

## RMS <sup>Value</sup> ~~Power~~

The value of a DC source if it were to supply a power equal to the average power supplied by the AC source [and similar for non-sources]. → Effective / RMS value.

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V(t))^2 dt}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T (I(t))^2 dt}$$

For sinusoids (single phase), [sine, cosine]

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

Where,  $V(t) = V_m \sin(\omega t + \theta_v)$  for cos

$I(t) = I_m \cos(\omega t + \theta_i)$  for sin


□ Can be used in all DC formulas.

## Apparent Power

Let,

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$I(t) = I_m \cos(\omega t + \theta_I)$$

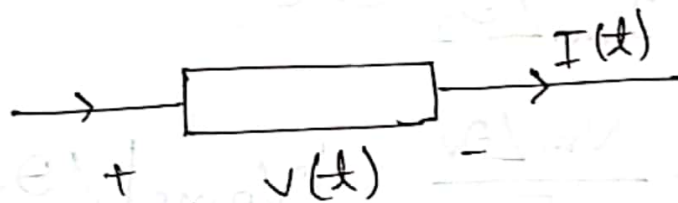

$$|V_{rms}| = \frac{V_m}{\sqrt{2}} \quad , \quad |I_{rms}| = \frac{I_m}{\sqrt{2}}$$

$\square \text{ Apparent Power} = |V_{rms}| \cdot |I_{rms}|$

## Power Factor

↳ Cosine of the phase difference voltage and current / Load angle.

$$\therefore \boxed{pf = \cos(\theta_v - \theta_I)} = \cos(\theta_{load})$$

## Complex Power $\boxed{S}$

Let,

$$V(t) = V_m \cos(\omega t + \theta_v) \quad \text{--- } \cancel{V_{rms} \angle \theta_v}$$
$$= V_m \angle \theta_v$$

$$I(t) = I_m \cos(\omega t + \theta_i)$$
$$= I_m \angle \theta_i$$

$$\therefore V_{rms} = \frac{V_m \angle \theta_v}{\sqrt{2}} = |V_{rms}| \angle \theta_v$$

$$I_{rms} = \frac{I_m \angle \theta_i}{\sqrt{2}} = |I_{rms}| \angle \theta_i$$

~~Complex Power =  $V_{rms} \cdot I_{rms}$~~

$\square \text{ Complex Power, } S = |V_{rms}| \cdot |I_{rms}| \angle \theta_v - \theta_i$

$$= P + jQ$$
$$= V_{rms} \cdot I_{rms}^*$$

Here,

$P \rightarrow$  Real Power

$Q \rightarrow$  Reactive Power



Real Power

Complex Power

$$P = \operatorname{Re}(S) = S \cos(\theta_v - \theta_i)$$

- Resistance absorbs Real power.

Reactive Power

$$Q = \operatorname{Im}(S) = S \sin(\theta_v - \theta_i)$$


- Capacitance, Inductance

↓  
Reactive Power

↓  
Neither supply nor dissipate power,  
actually, but exchange power back and forth,

## Examples Power

Sadiku → 11.11

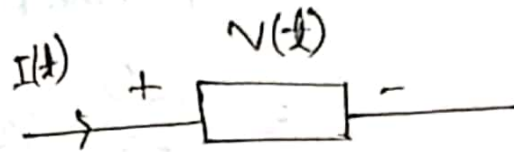

$$V(t) = 60 \cos(\omega t - 10^\circ) \text{ V}$$

$$I(t) = 1.5 \cos(\omega t + 50^\circ) \text{ A}$$

a)  $\text{Complex Power} = |V_{\text{rms}}| |I_{\text{rms}}| \angle \theta_v - \theta_i$

Here,  $\theta_v = -10^\circ$

$\theta_i = 50^\circ$

$$|V_{\text{rms}}| = \frac{V_m}{\sqrt{2}} = \frac{60}{\sqrt{2}}$$

$$|I_{\text{rms}}| = \frac{I_m}{\sqrt{2}} = \frac{1.5}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ$$

$$I_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle 50^\circ$$

$$\begin{aligned} \therefore \text{Complex Power, } S &= V_{\text{rms}} \cdot I_{\text{rms}}^* \\ &= \frac{60}{\sqrt{2}} \cdot \frac{1.5}{\sqrt{2}} \angle -10^\circ - 50^\circ \\ &= \boxed{45 \angle -60^\circ \text{ VA}} \end{aligned}$$

(mm.)

$$\begin{aligned}\text{Apparent Power} &= |V_{rms}| |I_{rms}| \\ &= \frac{60}{\sqrt{2}} \times \frac{1.5}{\sqrt{2}} \text{ VA} \\ &= \boxed{45 \text{ VA}}\end{aligned}$$

$$\text{b) } S = 45 \angle -60^\circ = 22.5 - j38.97$$

$\swarrow$   $P$                        $\searrow$   $Q$

$$\therefore \text{Real Power} = \boxed{22.5 \text{ W}}$$

$$\text{Reactive Power} = \boxed{-38.97 \text{ VAR}}$$

$$\begin{aligned}\text{c) } \text{pf} &= \cos(-10^\circ - 50^\circ) = \cos(-60^\circ) \\ &= \boxed{0.5} \text{ (leading)}\end{aligned}$$

$$\text{Load Impedance, } Z = \frac{V}{I}$$

$\downarrow$  Current ahead

$$= \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ} = \boxed{40 \angle -60^\circ \Omega}$$

$\swarrow$  (Ans)  
Capacitive




## Superposition

in AC

- Important when frequency different in different sources
- Similar Concept as DC.

Example

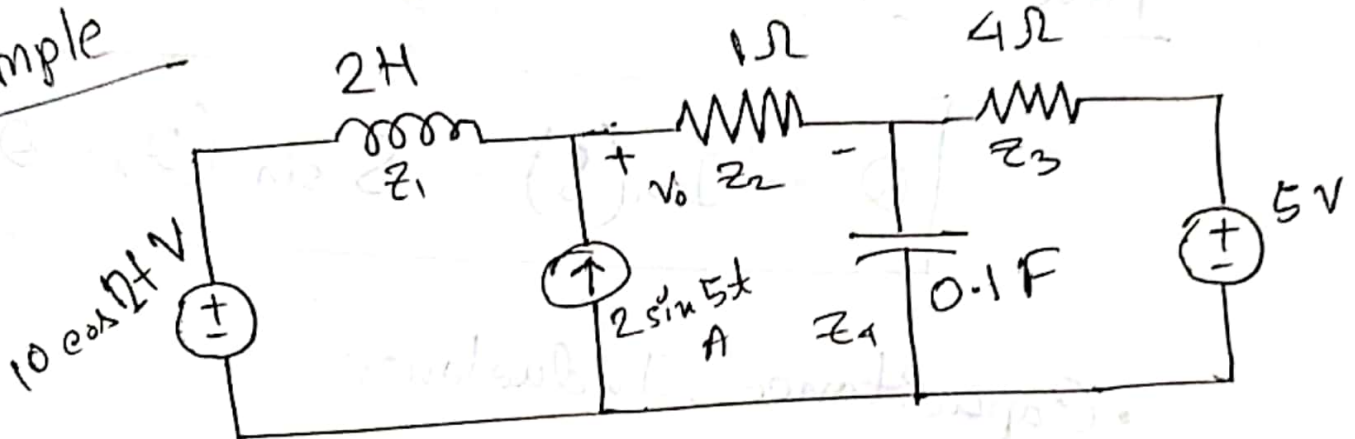


$$Z_1 = j\omega L = j\omega?$$

↳ Different  $\omega$ .

Superposition needed.

$$\therefore V_0 = V_1 + V_2 + V_3 \quad \text{One for each source!}$$

10 cos 2t V source On

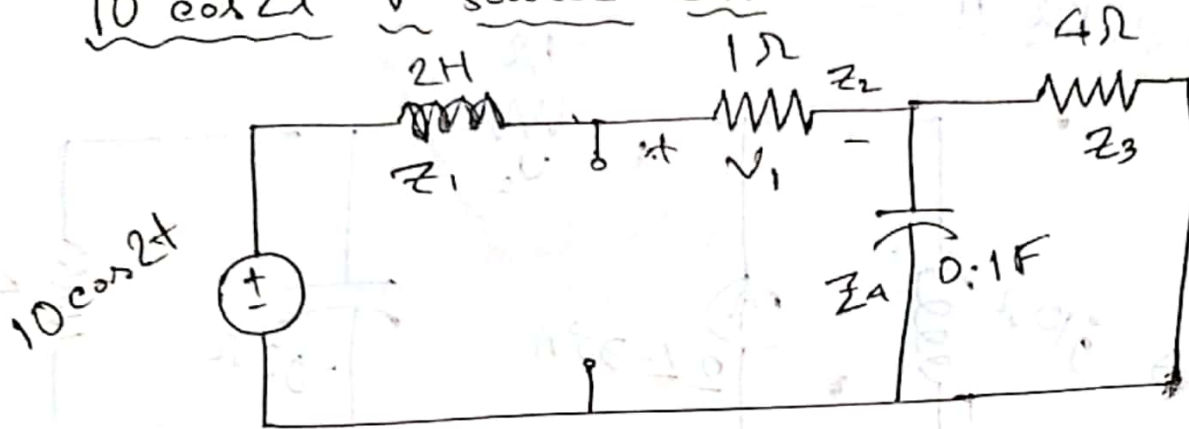

$$Z_1 = j\omega L = j \times 2 \times 2 = 4j$$

$$Z_4 = \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 0.1} = -5j$$

$$10 \cos 2t \rightarrow 10 \angle 0^\circ \text{ V}$$

$$\therefore V_1 = 10 \angle 0^\circ \times \frac{Z_2}{Z_1 + Z_2 + Z_3 \parallel Z_4}$$

| Voltage Divided |

$$= 10 \angle 0^\circ \times \frac{1}{4j + 1 + (-35j \parallel 4)}$$

$$= 10 \angle 0^\circ \times \frac{1}{4j + 1 + \frac{-35 \times 4}{4 - 35}}$$


$$= 2.439 - j1.951$$

$$= 2.498 \angle -30.79^\circ$$

$$\therefore V_1(t) = 2.498 \cos(2t - 30.79^\circ)$$

$2 \sin 5t$  A Source


Using  $\omega = 5$

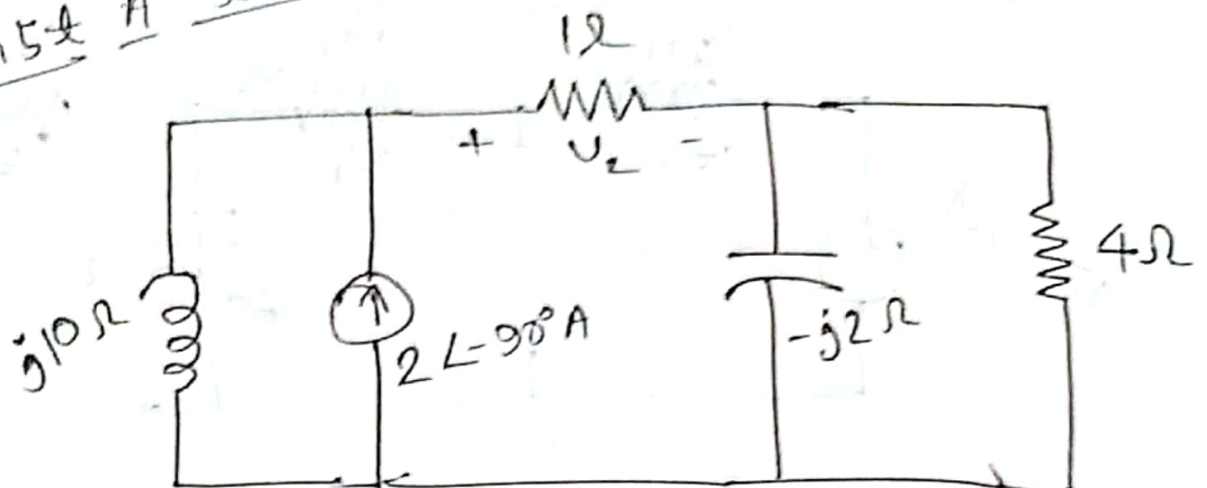

Performing Similar Analysis,

$$V_2 = 2.33 \cos(5t - 80^\circ)$$

5V source

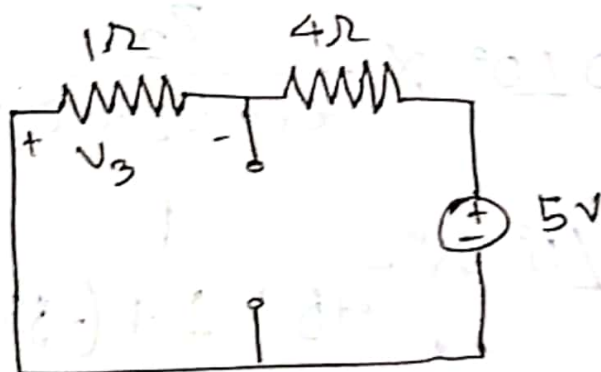

DC circuit  
 $\downarrow$   
 $\sim \sim \sim \rightarrow$  Short  
 $-||-$  Open

$$\therefore V_3 = - \frac{1}{1+4} \times 5$$

$$= -1 \text{ V}$$

$$\therefore V_0 = V_1 + V_2 + V_3 = 2.498 \cos(2t - 30.79^\circ) + 2.33 \cos(5t - 80^\circ) - 1 \text{ V}$$