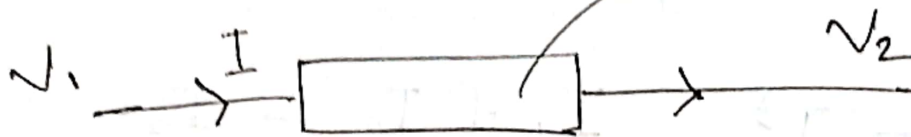


Week - 4

Nodal Analysis

Reviews

Resistance & Ohm's Law



Ohm's Law  $\rightarrow I \propto \Delta V$   
 $\Rightarrow I \propto V_1 - V_2$

Now,  $I \propto \Delta V$

$\Rightarrow I = G \Delta V$

$G = \frac{1}{R}$


$R = \frac{1}{G}$  Unit: Ohm ( $\Omega$ )

How much it will resist current.

$\therefore I = \frac{\Delta V}{R}$



KCL

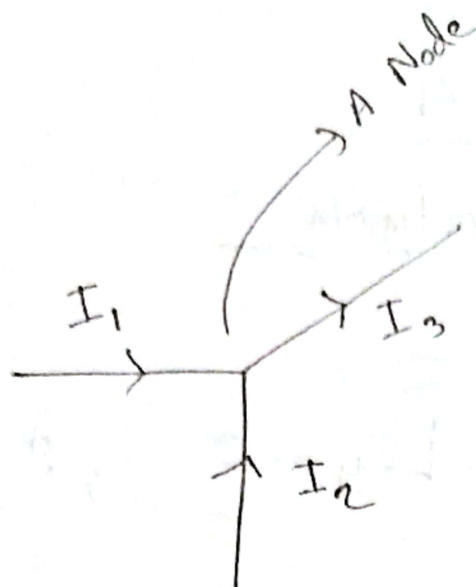

All currents entering



$$\sum I = 0$$

KCL


$$I_1 + I_2 = I_3$$

Total in = Total out

Example:

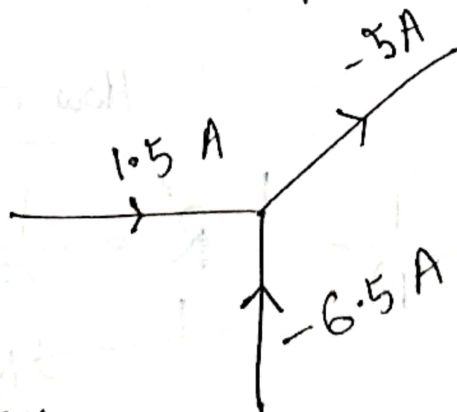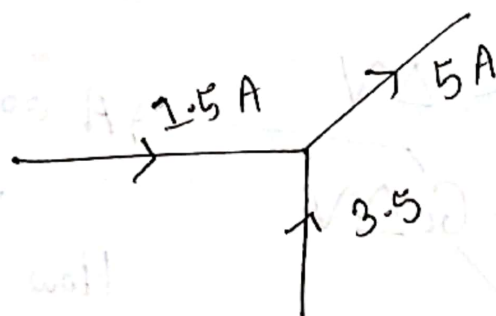

$\Rightarrow$

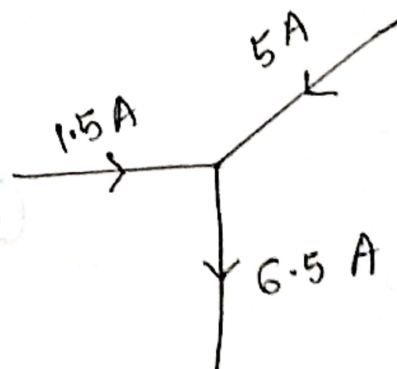



Passive  
Sign Convention

Current entering the Node  $\rightarrow$  Add

Current exiting the Node  $\rightarrow$  Subtract


Nodes

Connects two/more electric components

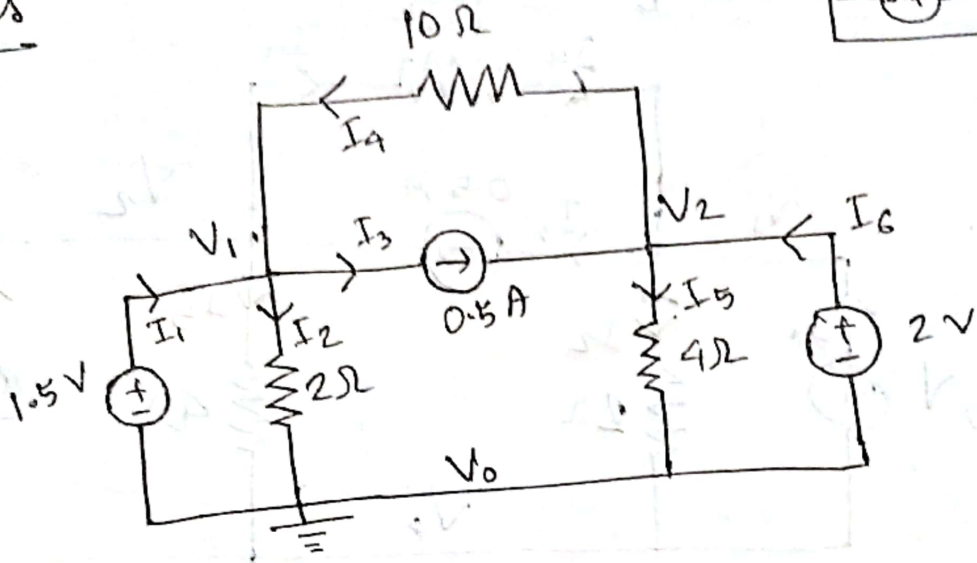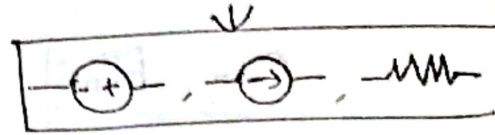


Finding Out Nodes


No components in between

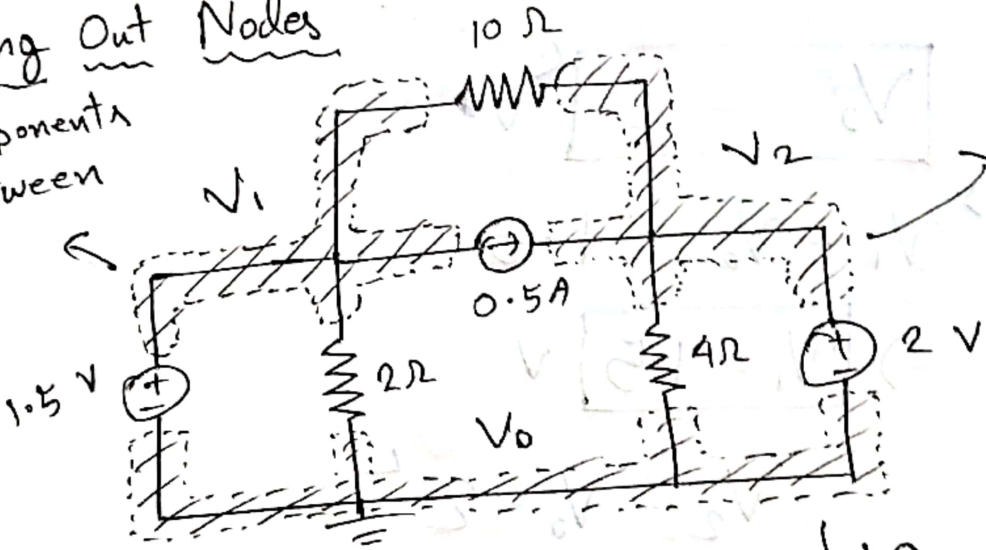

Same voltage in all points

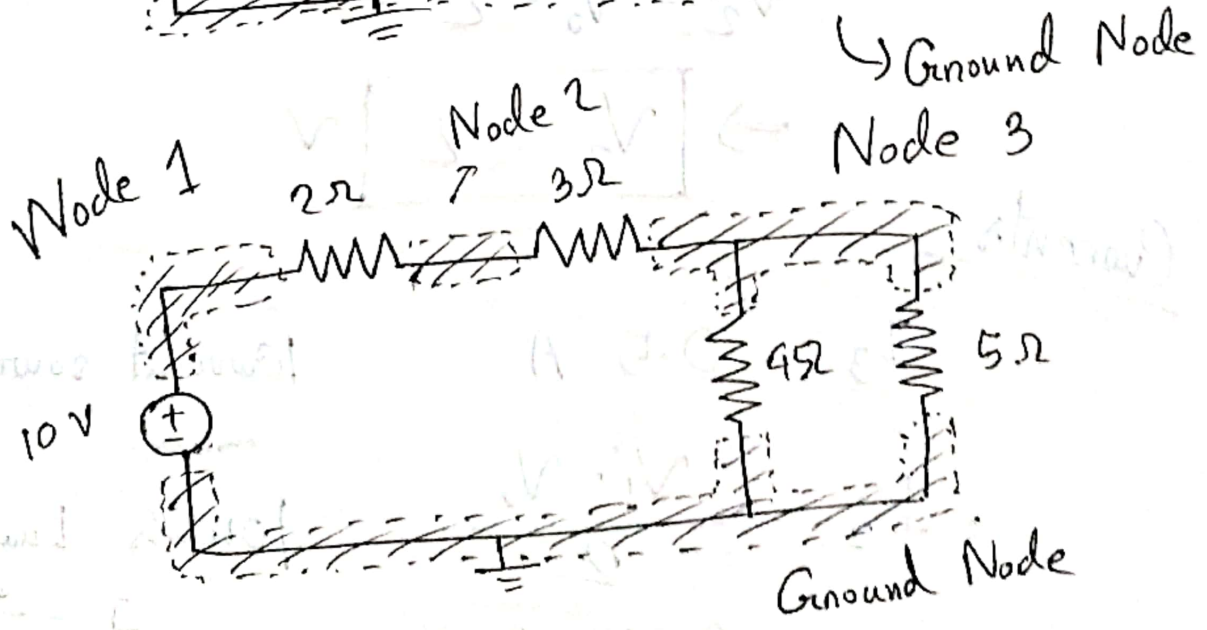

## Our First Analysis

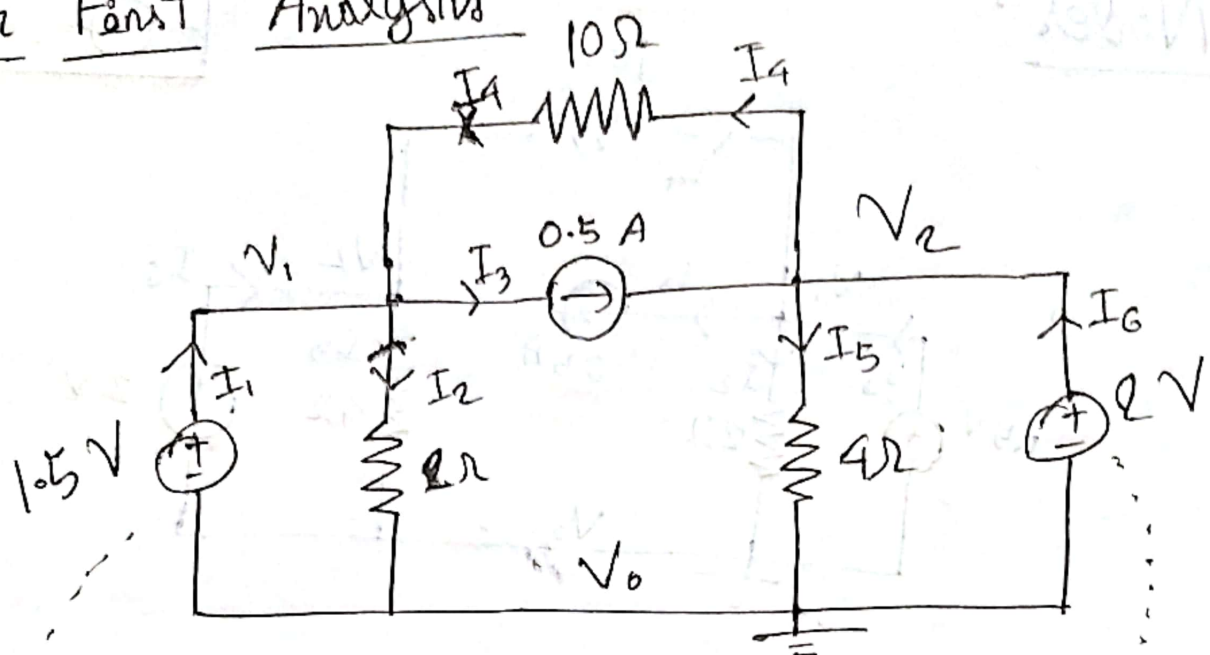

Voltages

$$\boxed{V_0 = 0} \text{ V}$$

$$V_1 - V_0 = 1.5$$

$$\Rightarrow \boxed{V_1 = 1.5} \text{ V}$$

$$V_2 - V_0 = 2$$

$$\Rightarrow \boxed{V_2 = 2} \text{ V}$$

Currents

$$I_3 = 0.5 \text{ A}$$

|Current source|

$$I_2 = \frac{V_1 - V_0}{2}$$

$$= 0.75 \text{ A}$$

|Ohm's Law,

$$I = \frac{\Delta V}{R} \quad |$$

$$I_4 = \frac{V_2 - V_1}{10}$$

$$= \frac{2 - 1.5}{10}$$


$$= 0.05 \text{ A}$$

Ohm's law,

$$I = \frac{\Delta V}{R}$$

$I_1 = ? \Rightarrow$  Here comes KCL

For Node 1,

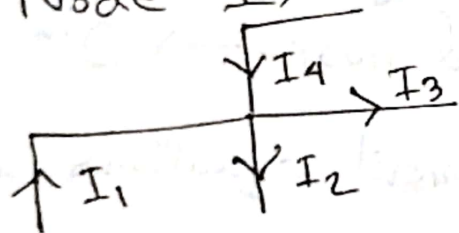

$\Rightarrow$  Entering Node 1  
 $\hookrightarrow I_4, I_1$   
 Exiting Node 1  
 $\hookrightarrow I_2, I_3$

$$\therefore -I_1 + I_2 + I_3 + I_4 = 0$$

$$\Rightarrow I_1 + I_4 = I_2 + I_3$$

$$\Rightarrow I_1 = I_2 + I_3 - I_4$$

$$= \boxed{1.2 \text{ A}}$$

[Solved]  $\rightarrow$  Try finding  $I_5, I_6$ .



## Nodal Analysis

↳ Goal: Finding all Node voltages using KCL & co.


## Steps

Step-1: Identifying all the nodes and marking them from 0 to N

[Ground node  $\rightarrow$  0<sup>th</sup> node]


Step-2: Write Component equations for all the voltage sources.

[Voltage difference = labeled value]

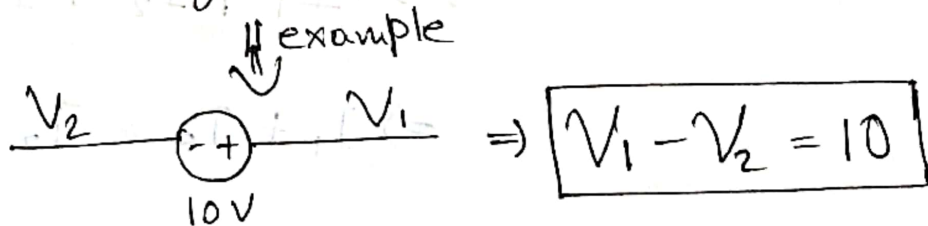

Step-3: Write the current through the resistors using Ohm's law,  $I = \frac{\Delta V}{R}$ . Passive

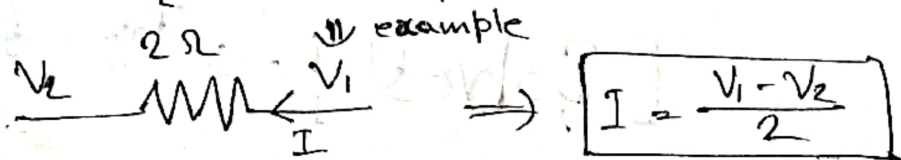[Direction as per wish, but must follow sign convention]



Step-4: Write KCL equations for all the nodes and supernodes with unknown Voltage.


[not needed <sup>↓</sup> in case of nodes with known  $V$  value]

Step-5: Solve all the equations to find all the <sup>node</sup> voltages.


[Calculation <sup>↓</sup> is useful]

# Nodal Analysis

1

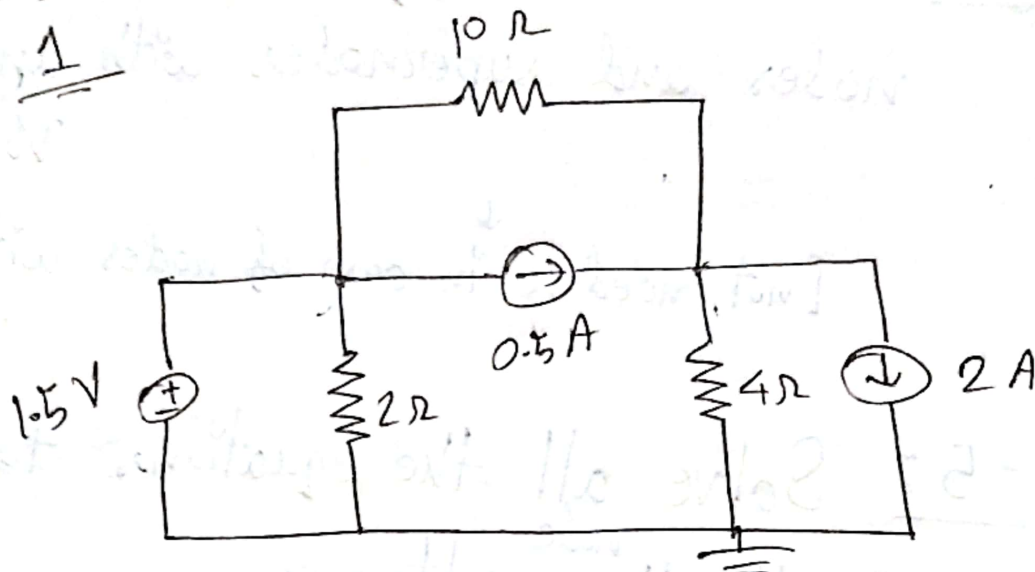

Step-1

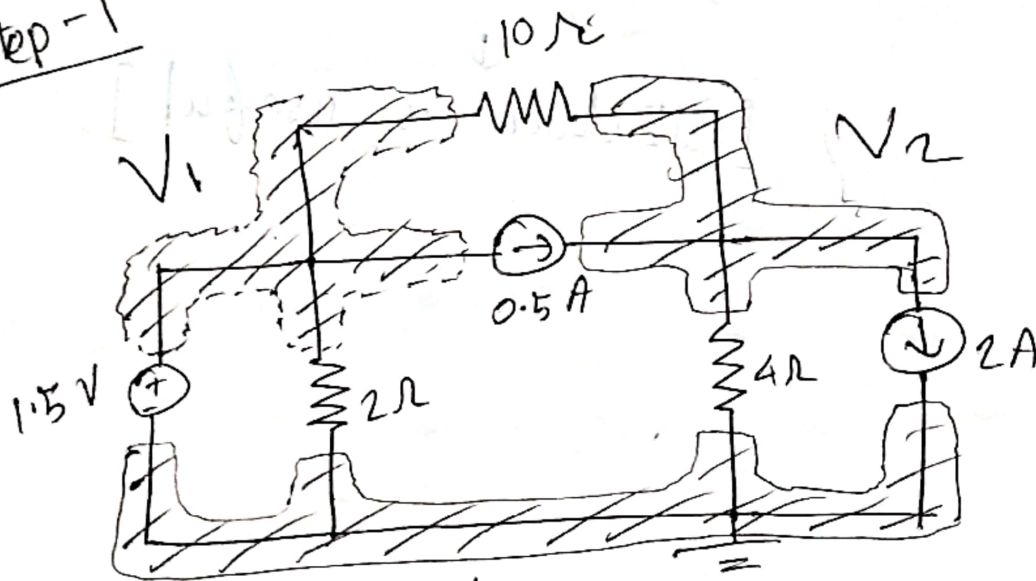

$$V_0 \rightarrow V_0 = 0V$$


Step-2

$$V_1 - V_0 = 1.5$$

$$\Rightarrow \boxed{V_1 = 1.5} V \quad \dots \quad (1)$$



Step-3

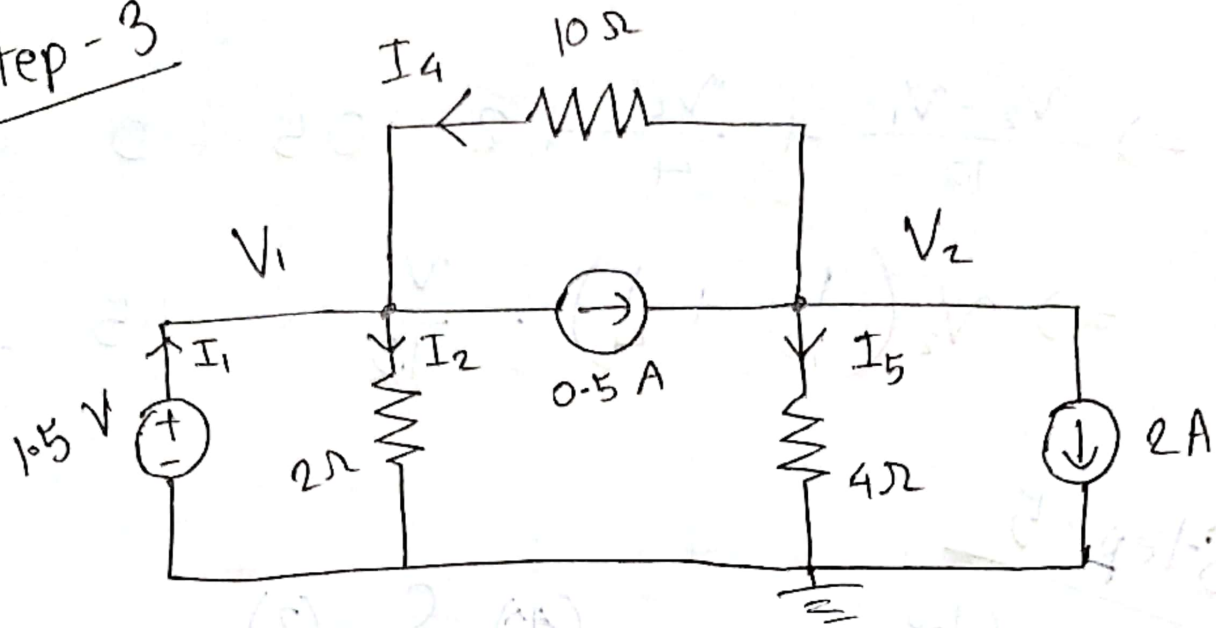

$$I_4 = \frac{V_2 - V_1}{10}$$

$$I_2 = \frac{V_1 - V_0}{2} = \frac{V_1}{2}$$

$$I_3 = \frac{V_2 - V_0}{4} = \frac{V_2}{4}$$

Step-4

Node 1  $\rightarrow V_1 = 1.5 \text{ V}$

No need to use KCL  $\rightarrow$  Already Known voltage.

Node 2

0.5  $\rightarrow$  Entering

2,  $I_4$ ,  $I_5$   $\rightarrow$  Exiting

$$\therefore I_4 + I_5 + 2 - 0.5 = 0$$

$$\Rightarrow \frac{V_2 - V_1}{10} + \frac{V_2}{4} + 2 - 0.5 = 0$$

$$\Rightarrow V_2 \left( \frac{1}{10} + \frac{1}{4} \right) - \frac{V_1}{10} = -1.5 \quad \text{--- (2)}$$

Step: 5

Using eqn. (1) & (2),

$V_1 = 1.5 \text{ V}$ $V_2 = -3.86 \text{ V}$
---

Using  
calculation



Can be used to answer any questions.

Current through  
4Ω?

$$\begin{aligned}
 I_5 &= \frac{V_2 - 0}{4} \\
 &= \frac{(-3.86) - 0}{4} \\
 &= -0.965 \text{ A}
 \end{aligned}$$

How much  
power consumed  
by 10  $\Omega$

$$P = \Delta V I = I^2 R = \frac{\Delta V^2}{R}$$

$$P = \frac{(V_2 - V_1)^2}{R}$$

$$= \frac{(-3.86 - 1.5)^2}{10}$$

$$= 2.87 \text{ W}$$

How much  
power connect  
source 2A  
supplying/consuming

$$P = \Delta V I$$

$$= (V_2 - V_0) \times 2$$

$$= (-3.86 - 0) \times 2$$

$$= -7.72 \text{ W}$$

↳

Negative  $\rightarrow$  Not  
consuming  $\rightarrow$  Supplying

How much  
power 1.5 V source  
consuming/supplying

$$P = \Delta V I$$
$$= 1.5 \times I_1$$

Using KCL,

$$I_1 + I_4 = I_2 + 0.5$$

$$\Rightarrow I_1 = I_2 + 0.5 - I_4$$

$$= \frac{1.5}{2} + 0.5 - \frac{-3.86 - 1.5}{10}$$

$$= -1.486 \text{ A}$$


$$\therefore P = 1.5 \times (-1.486) \text{ W}$$

$$= -2.23 \text{ W}$$

→ Supplying Power  
(-ve)
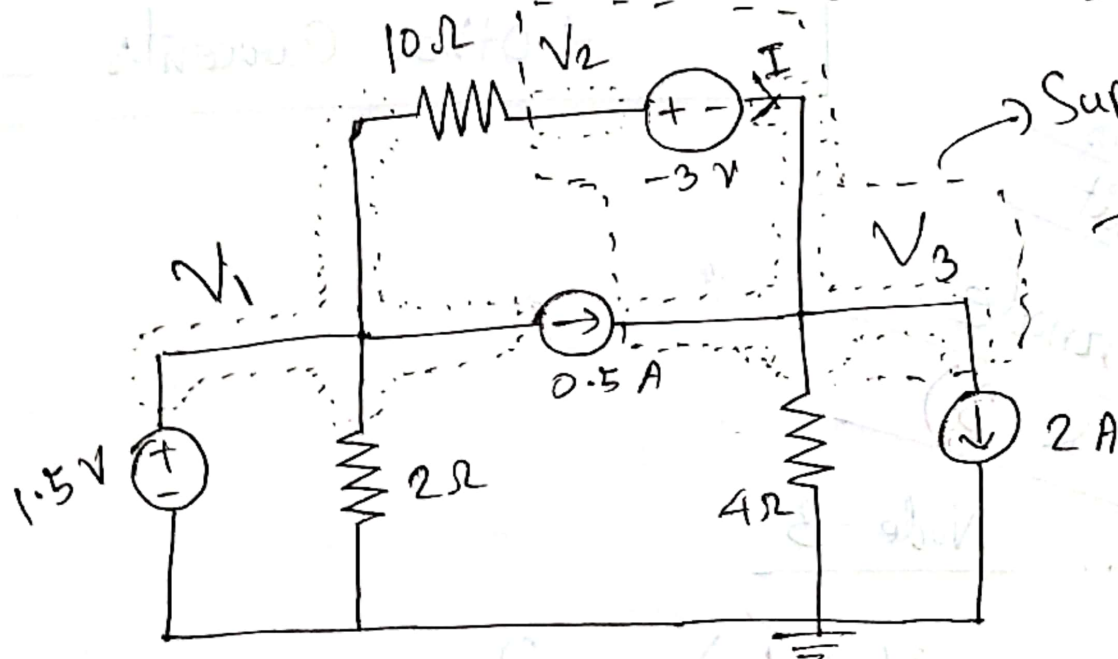
## Nodal Analysis 2

Supernode  $\rightarrow$  A voltage source between two non-ground nodes  $\Rightarrow$  A floating Voltage Source becomes **Supernode**



Step-2

$$V_1 = 1.5 \quad \text{--- (1)}$$

$$\underbrace{V_2 - V_3}_{\text{Supernode}} = -3 \quad \text{--- (2)}$$



Shortcut  
to Step-4

→ See Previous Example too!

$$V_2 \left( \begin{array}{l} \text{sum of} \\ \text{inverse of all resistances} \\ \text{connected to node-2} \end{array} \right)$$

$$- \frac{V_{\text{other side of resistance}}}{\text{resistance}} \left( \begin{array}{l} \text{inverse of resistance} \end{array} \right)$$

$$+ \text{Other currents} = 0$$

In this  
Circuit

Supernode  
(2 & 3)

Node-3

$$V_3 \left( \frac{1}{4} \right) - \frac{0}{4} + 2 - 0.5 - I = 0 \quad \text{--- (a)}$$

Node-2

$$V_2 \left( \frac{1}{10} \right) - \frac{V_1}{10} + I = 0 \quad \text{--- (b)}$$

$$(a) + (b) \Rightarrow V_3 \left( \frac{1}{4} \right) + V_2 \left( \frac{1}{10} \right) - \frac{0}{4} - \frac{V_1}{10} + 2 - 0.5 = 0 \quad \text{--- (3)}$$

Step-5

$$(1) \rightarrow V_1 = 1.5$$

$$(2) \rightarrow V_2 - V_3 = -3$$

$$(3) \rightarrow V_3\left(\frac{1}{4}\right) + V_2\left(\frac{1}{10}\right) - \frac{V_1}{10} - \frac{0}{4} + 2 - 0.5 = 0$$

$\Downarrow$  Solution


$$V_1 = 1.5 \text{ V}$$

$$V_2 = -6 \text{ V}$$

$$V_3 = -3 \text{ V}$$

(Ans.)

# □ Nodal Analysis

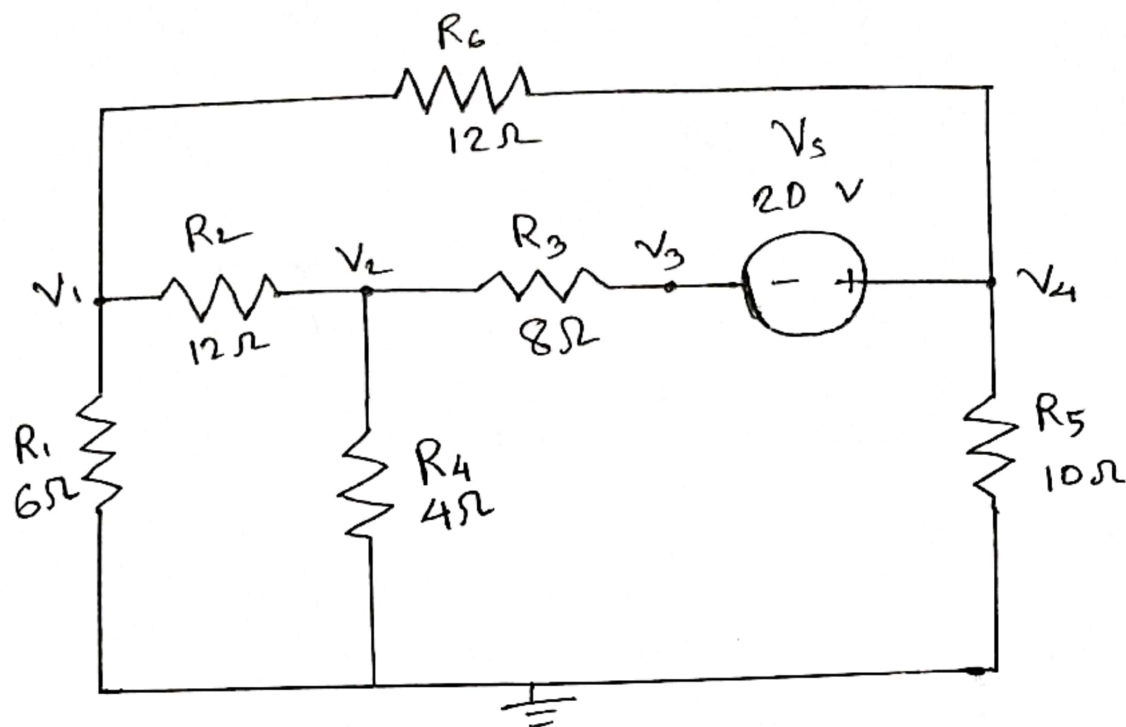

Node 1

Using KCL,

$$\frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_4}{R_6} = 0$$

$$\Rightarrow V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_6} \right) - \frac{V_2}{R_2} - \frac{V_4}{R_6} = 0$$

In this circuit  $\Rightarrow V_1 \left( \frac{1}{6} + \frac{1}{12} + \frac{1}{12} \right) - \frac{V_2}{12} - \frac{V_4}{12} = 0$

Node 2

$$\frac{V_2}{R_4} + \frac{V_2 - V_1}{R_2} + \frac{V_2 - V_3}{R_3} = 0$$

$$\Rightarrow V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{V_1}{R_2} - \frac{V_3}{R_3} = 0$$

$$\Rightarrow V_2 \left( \frac{1}{12} + \frac{1}{8} + \frac{1}{4} \right) - \frac{V_1}{12} - \frac{V_3}{8} = 0$$

# Common Mistake: Using  $-\frac{V_1}{R_1}$  instead of  $-\frac{V_1}{R_2}$ .

## SuperNode

Node 3

$$\frac{V_3 - V_2}{R_3} - I = 0 \quad \dots \dots (1)$$

Node 4

$$\frac{V_4}{R_5} + \frac{V_4 - V_1}{R_6} + I = 0 \quad \dots \dots (2)$$

Component Equation  $\Rightarrow V_4 - V_3 = V_s$

In this circuit  $\Rightarrow V_4 - V_3 = 20$

|Answer of Ques. 3|

$\therefore$  Supernode Eqn.  $\Rightarrow (1) + (2)$  |At Node 3 and 4|

$$\Rightarrow \frac{V_3}{R_3} + \cancel{V_4} \left( \frac{1}{R_5} + \frac{1}{R_6} \right) - \frac{V_1}{R_6} - \frac{V_2}{R_3} = 0$$

$$\text{In this circuit, } \Rightarrow \frac{V_3}{8} + V_4 \left( \frac{1}{10} + \frac{1}{12} \right) - \frac{V_1}{12} - \frac{V_2}{8} = 0$$

|Answer of Ques. 4|

### Common Mistakes:

1) Writing separate Node 3, 4 equations but not putting  $-I, +I$  in them. Remember, The eqn. is incomplete without them.

2) Using  $-\frac{V_1}{R_1}$  instead of  $-\frac{V_1}{R_6}$ .

## Power

Solving for  $V_1, V_2, V_3, V_4$  from the 4 equations,

$$V_1 = 0.897 \text{ V}$$

$$V_2 = -3.34 \text{ V}$$

$$V_3 = -13.02 \text{ V}$$

$$V_4 = 6.98 \text{ V}$$

Now, from Node -3 eqn.,  $\frac{V_3}{R_3} - \frac{V_2}{R_3} - I = 0$

$$\Rightarrow I = \frac{V_3}{R_3} - \frac{V_2}{R_3}$$

$$\therefore P = VI = V_s I$$

In this circuit,

$$I = \frac{-13.02}{8} + \frac{3.34}{8}$$
$$= -1.204 \text{ A}$$

$$\therefore P = 20 \times (-1.204)$$

$$= -24.08 \text{ W}$$

Common Mistake: Taking the sign of  $I$

wrong. Results in  $P$  becoming a positive value. Wrong according to passive sign convention which shows whether it's supplying or consuming power.