Student ID:	22301061	Lab Section:	22
Name:	Faiaz Abrar Zaman Apoy	Lab Group:	06

Experiment No. 3

Verification of Superposition Principle

Objective

The aim of this experiment is to experimentally verify the Superposition theorem, which is an analytical technique for determining currents/voltages in a circuit with more than one emf source.

Theory

The Superposition Principle is a fundamental concept in electrical circuits that states that in any linear, active, bilateral network having more than one source, the response across any element is the sum of the responses obtained from each source considered separately, and all other sources are replaced by their internal resistance. The superposition theorem is used to solve networks where two or more sources are present and connected. The current or voltage through any component in a circuit is the sum of the effects of each individual source acting alone. In other words, the principle states that **the total response of a circuit with multiple sources is the sum of the responses of the circuit to each individual source acting alone.** This principle is widely used in circuit analysis to simplify complex circuits and solve them with ease.

In a **linear circuit** containing multiple independent sources and linear elements (e.g., resistors, inductors, and capacitors), the voltage across (or the current through) any element when all the sources are acting simultaneously may be obtained by adding algebraically all the individual voltages (or currents) caused by each independent source acting alone, with all other sources deactivated.

An independent **voltage source** is deactivated (made zero) by **shorting** it, and an independent **current source** is deactivated (made zero) by **open circuiting** it. However, if a dependent source is present, it must remain active during the superposition process.

Apparatus

- Multimeter
- Resistors ($1\ k\Omega,\ 2.2\ k\Omega,\ 3.3\ k\Omega$).
- DC power supply
- Breadboard
- Jumper wires

Procedures

- Measure the resistances of the provided resistors and fill up the data table (Table 1).
- Construct the following circuit on a breadboard. Try to use minimum number of jumper wires:

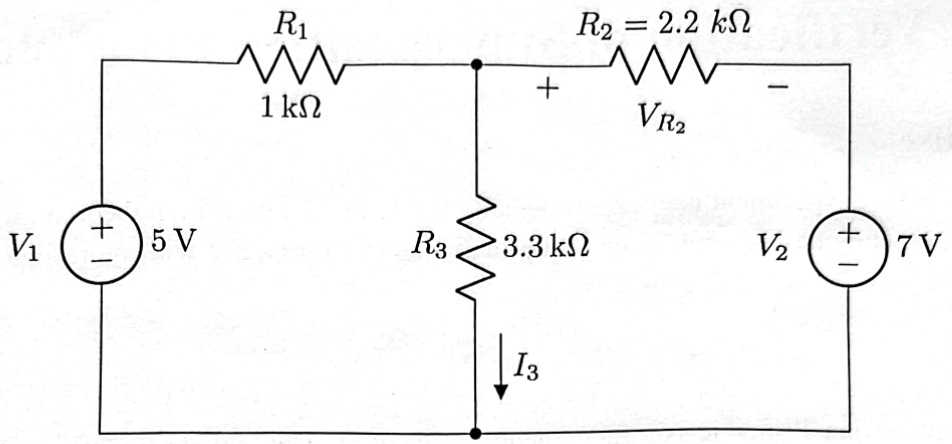

Circuit 1

- Measure the voltage across the resistors R_2, R_3 and current through the resistor R_3. Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3) through R_3. Fill up the data tables.
- Render V_1 inactive (keeping V_2 active) and construct the following circuit.

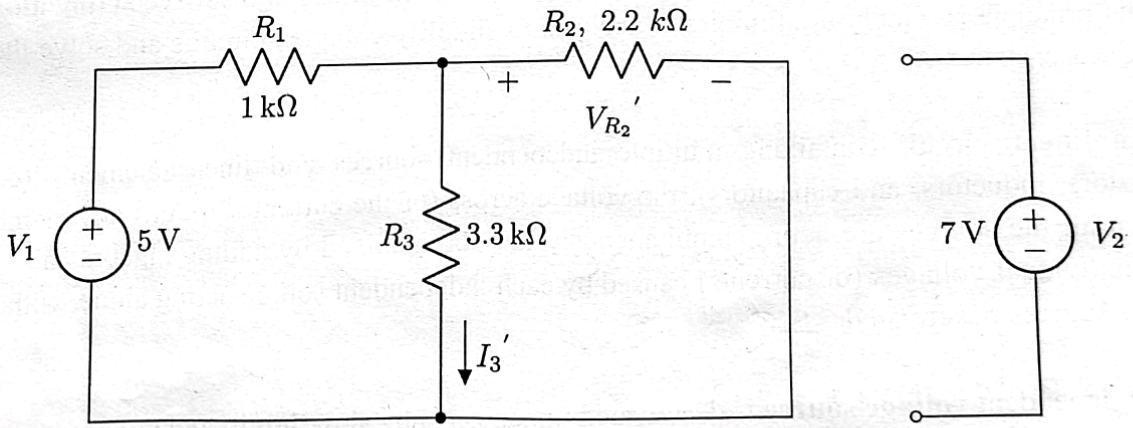

Circuit 2

- Measure the voltage across the resistors R_2, R_3 and current through the resistor R_3. Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3') through R_3. Fill up the data tables.
- Render V_2 inactive (keeping V_1 active) and construct the following circuit.

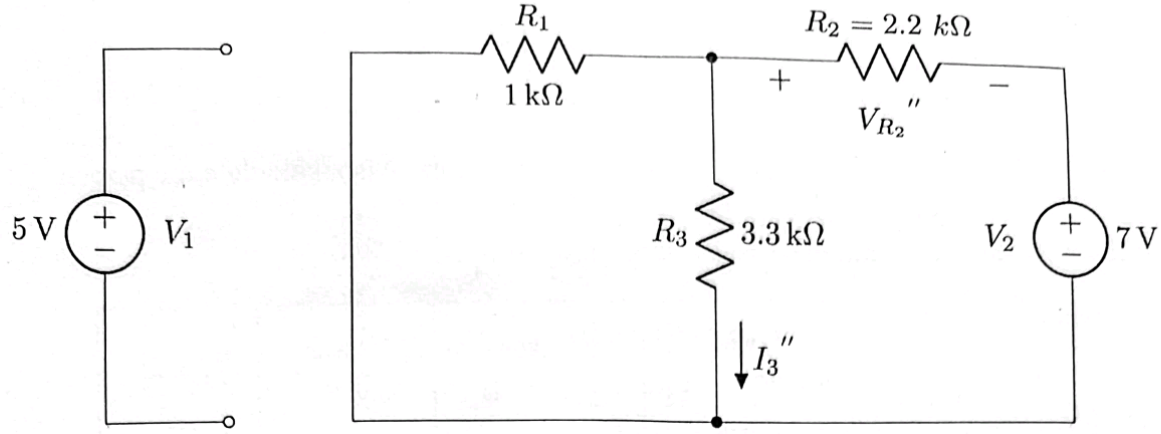

Circuit 3

- Measure the voltage across the resistors R_2, R_3 and current through the resistor R_3. Use a Multimeter for measuring the voltage and use Ohm's law to calculate the current (I_3'') through R_3. Fill up the data tables.
- Verify if $I_3 = I_3' + I_3''$ which would validate the superposition theorem for the current through R_3.
- Verify if $V_{R_2} = V_{R_2}' + V_{R_2}''$ which would validate the superposition theorem for the voltage across R_2.

Data Tables

Signature of Lab Faculty: **Date:**

** ***For all the data tables, take data up to three decimal places, round to two, then enter into the table.***

Table 1: Resistance Data

For all your future calculations, please use the observed values only **(even for theoretical calculations)**.

Notation	Expected Resistance	Observed Resistance (kΩ)
R_1	1 kΩ	0.98
R_2	2.2 kΩ	2.15
R_3	3.3 kΩ	3.25

Table 2: Current through R_3 and voltage across R_2

In the following table, I_3 is the current through R_3 and V_{R_2} is the voltage drop across the resistor R_2. Similar syntax applies to the remaining resistors. Also, calculate the percentage of error between expected and observed values of $I_3^{'} + I_3^{''}$.

Observation	I_3 with both V_1 and V_2 active (mA)	$I_3^{'}$ with only V_1 is active (mA)	$I_3^{''}$ with only V_2 is active (mA)	$I_3^{'} + I_3^{''}$ (mA)
Experimental	1.44	0.87	0.55	1.43
Theoretical	1.42	0.86	0.54	1.4
Observation	V_{R_2} with both V_1 and V_2 active (V)	$V_{R_2}^{'}$ with only V_1 is active (V)	$V_{R_2}^{''}$ with only V_2 is active (V)	$V_{R_2}^{'} + V_{R_2}^{''}$ (V)
Experimental	−2.36	2.83	−5.19	−2.36
Theoretical	2.351	−2.89	5.2	2.37

- **Percentage of error** $= \left|\frac{Observed\ Value - Expected\ Value}{Expected\ Value}\right| \times 100\%$

N.B: Here, the Expected values are I_3, V_{R_2} *and the Observed values are* $I_3^{'} + I_3^{''}$ *and* $V_{R_2}^{'} + V_{R_2}^{''}$ respectively.

Hence, Percentage of error in $I_3^{'} + I_3^{''}$ calculation = $\boxed{0.694\ \%}$

Hence, Percentage of error in $V_{R_2}^{'} + V_{R_2}^{''}$ calculation = $\boxed{0.425\ \%}$

Questions

1. Calculate the **power associated** with R_2 using the experimentally measured values of currents or voltages when:

   - Only V_1 source is active.
   - Only V_2 source is active.
   - Both V_1 and V_2 sources are active.

   Fill out the Table given below and verify, whether the superposition theorem is verified or not in this case. If not, comment on the reasons. **You don't need to take any new readings for this task.** Use previous data from Table 2 to calculate the power. Remember, power consumed by a resistor, $P = VI = I^2R = \frac{V^2}{R}$

Observation	P_{R_2} when both V_1 and V_2 active $P_{R_2} = \frac{V_{R_2}^2}{R_2}$ (W)	P_{R_2}' when only V_1 is active $P_{R_2}' = \frac{V_{R_2}'^2}{R_2}$ (W)	P_{R_2}'' when only V_2 is active $P_{R_2}'' = \frac{V_{R_2}''^2}{R_2}$ (W)	$P_{R_2}'+P_{R_2}''$ (W)
Experimental	2.59	3.125	12.528	16.253
Theoretical	2.512	3.640	12.29	15.93

Is the Superposition Principle applicable in the case of Power?

☐ Yes ☑ No

How would you relate your findings from this to the concept of linearity? Why does/doesn't it work when it comes to Power?

The superposition principle is not directly applicable to power because power is not a linear quantity. The concept of linearity is applicable for current and voltage but not for power.

2. Why was a short circuit wire required to be connected between the corresponding terminals while turning off a voltage source? Why wasn't simply turning off the power switch enough to deactivate the source?

This is because the voltage source may have its own resistance even when switched off, so we use short circuit wire instead. It also ensures safe dissipation of residual electrical energy and prevents potential hazards. Just turning off the power switch may not be enough to deactivate a source completely.

3. For the circuit shown below,

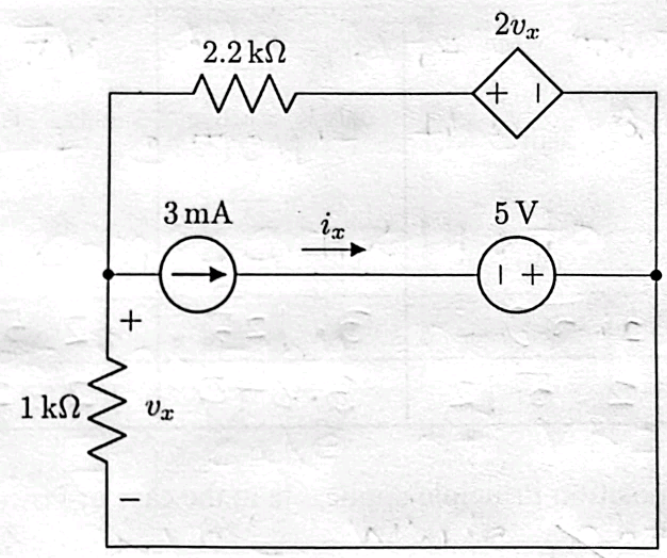

(a) Show using the Superposition Principle that the 5 V voltage source has no effect on the current i_x.

$$+2V_{x_1} - V_{x_1} - 2.2 i_1 \times 10^3 = 0$$

$$\Rightarrow 2(i_1 \times 10^3) - i_1 \times 10^3 - 2.2 i_1 \times 10^3 = 0$$

$$\Rightarrow (2i_1 - i_1 - 2.2 i_1) \times 10^3 = 0$$

$$\Rightarrow i_1 = 0$$

The 5 V voltage has no effect on the current I_x

(b) Why the 5 V voltage source does not contribute to the current i_x?

The 5V voltage source does not contribute to the current Ix because of the infinite resistance of the current source and also both current and voltage are independent sources, so the circuit is not influenced by a particular voltage source

(c) Can you draw any conclusions about the resistances of an ideal voltage and current source from this? If so, what are they?

The ideal resistance of a current source is infinite and of a voltage source is zero. An ideal voltage (5V in the given circuit) source maintains a constant voltage to the circuit regardless of the current flowing through it. An ideal current source supplies a constant current regardless of the voltage across its terminal. An ideal current source doesn't matter connect with an voltage here in Ix

Report

1. Fill up the theoretical parts of all the data tables.
2. Answer to the questions.
3. Discussion *[your overall experience, accuracy of the measured data, difficulties experienced and your thoughts on those]*. Add pages if necessary.

Discussion:

Firstly, as a group we had to measure the actual value of the resistance given to us. And following this according to circuit 1; we had to plot the diagram on breadboard before taking data for table 2; We set the DC supply to 5V and 7V and later turned it off and short circuit the voltages 5V and 7V consecutively, to figure out the super position principle of the current. In case of VR_2 the process remained same. While obtaining results experimental and theoritical results are quite different due to the slight different measurement of the observed resistance particularly and physically it varies as the element contains their own resistance too.